

UNIT 1: BINARY SYSTEMS

esilichha.com Lincoln University

Digital Systems [?] Analog And Digital Signal [?]
Binary Numbers: Number-base Conversions : Octal
And Hex

esikhcha.com Lincoln University

Introduction to Digital Systems

Digital systems are essential frameworks that process, store, and communicate information in a digital format.

They consist of components such as processors, memory, and input/output devices that work together to perform various functions.

Understanding digital systems is crucial for fields such as computer science, telecommunications, and electronics.

Advantages of Digital Systems


- Digital systems are easier to design: As the circuits are mainly switching circuits, where exact values of voltage or current are not important. But only the range (HIGH or LOW) in which a specific voltage falls is important.
- Information storage is easy
- Accuracy and precision are greater: Digital systems can handle as many digits of precision as you need simply by adding more switching circuits. In Analog system precision is limited to only three or four digits.
- Operation can be programmed: digital system operations can be programmed more easily as the variety and complexity of the problem is limited compared to analog system operations.

Analog vs. Digital Signals

Analog signals are continuous signals that represent physical quantities, such as sound and light.

Digital signals, on the other hand, are discrete and represent information in binary form, using zeros and ones.

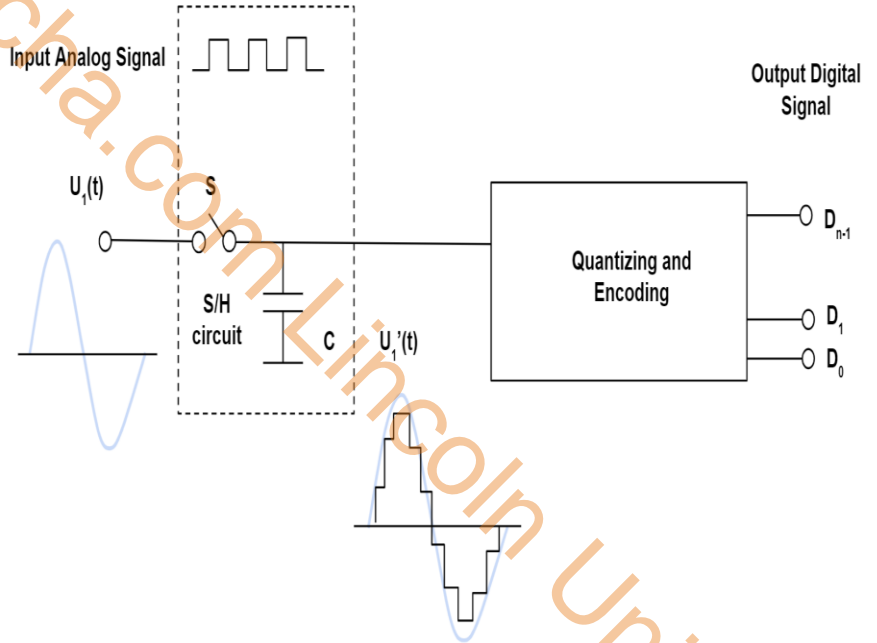The conversion from analog to digital signals allows for easier manipulation, storage, and transmission of data in modern technology.




Characteristics of Analog Signals

Analog signals can take on an infinite number of values within a given range, making them highly detailed.

They are susceptible to noise and distortion, which can degrade the quality of the signal over time.

 Common examples of analog signals include audio recordings and traditional television broadcasts.



Characteristics of Digital Signals

Digital signals represent data using binary code, making them less prone to error and easier to store.

They can be compressed and encrypted, providing enhanced security and efficiency for data transmission.

Examples of digital signals include computer data, digital audio, and video files.




Introduction to Binary Numbers

Binary numbers are the foundation of digital systems, utilizing only two digits: 0 and 1.

Every digital system operates on binary, as it aligns with the on-off states of electronic circuits.

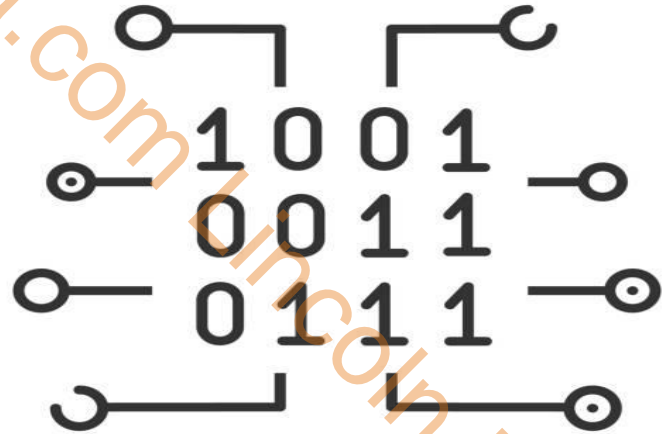Understanding binary numbers is essential for programming and digital circuit design.



Converting Decimal to Binary


To convert a decimal number to binary, divide the number by 2 and record the remainder.

Continue dividing the quotient by 2 until the quotient is zero, then read the remainders in reverse order.

This method allows for precise representation of decimal values in binary format.

Convert the following Decimal Number into Binary

201/2	100	1
100/2	50	0
50/2	25	0
25/2	12	1
12/2	6	0
6/2	3	0
3/2	1	1

 


Introduction to Octal Numbers

Octal numbers use a base-8 system, utilizing digits from 0 to 7 to represent values.

Each octal digit corresponds to three binary digits, facilitating easier human interpretation of binary data.

 Octal is less commonly used today but is still relevant in certain computing applications.



Decimal Number : 140

$$(140)_8 = (96)_{10}$$

Converting Binary to Octal

To convert binary to octal, group the binary digits into sets of three, starting from the right.

If necessary, add leading zeros to complete the leftmost group of three.

Each group can then be directly converted into its corresponding octal digit.



Introduction to Hexadecimal Numbers

Hexadecimal numbers operate on a base-16 system, using digits from 0 to 9 and letters A to F to represent values.

This system is more compact than binary and can represent larger values with fewer digits.

Hexadecimal is commonly used in programming and computer science to simplify binary representations.

HEXADECIMAL VALUES																DECIMAL RANGE
00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F	00-15
10	11	12	13	14	15	16	17	18	19	1A	1B	1C	1D	1E	1F	16-31
20	21	22	23	24	25	26	27	28	29	2A	2B	2C	2D	2E	2F	32-47
30	31	32	33	34	35	36	37	38	39	3A	3B	3C	3D	3E	3F	48-63
40	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D	4E	4F	64-79
50	51	52	53	54	55	56	57	58	59	5A	5B	5C	5D	5E	5F	80-95
60	61	62	63	64	65	66	67	68	69	6A	6B	6C	6D	6E	6F	96-111
70	71	72	73	74	75	76	77	78	79	7A	7B	7C	7D	7E	7F	112-127
80	81	82	83	84	85	86	87	88	89	8A	8B	8C	8D	8E	8F	128-143
90	91	92	93	94	95	96	97	98	99	9A	9B	9C	9D	9E	9F	144-159
A0	A1	A2	A3	A4	A5	A6	A7	A8	A9	AA	AB	AC	AD	AE	AF	160-175
B0	B1	B2	B3	B4	B5	B6	B7	B8	B9	BA	BB	BC	BD	BE	BF	176-191
C0	C1	C2	C3	C4	C5	C6	C7	C8	C9	CA	CB	CC	CD	CE	CF	192-207
D0	D1	D2	D3	D4	D5	D6	D7	D8	D9	DA	DB	DC	DD	DE	DF	208-223
E0	E1	E2	E3	E4	E5	E6	E7	E8	E9	EA	EB	EC	ED	EE	EF	224-239
F0	F1	F2	F3	F4	F5	F6	F7	F8	F9	FA	FB	FC	FD	FE	FF	240-255

Converting Binary to Hexadecimal

To convert binary to hexadecimal, group the binary digits into sets of four, starting from the right.

Similar to octal conversion, add leading zeros if necessary to complete the leftmost group.

Each group of four binary digits corresponds to a single hexadecimal digit, allowing for easy conversion.

Binary to Hexadecimal Conversion Table



Hexadecimal Number	Binary Number
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
A	1010
B	1011
C	1100
D	1101
E	1110
F	1111

**Complements ☐ Signed Binary Numbers ☐ Binary
Codes ☐ Binary Storage & Registers**

esikhcha.com Lincoln University

Introduction to Complements

Complements are fundamental in binary arithmetic and digital systems.

They allow for simplified subtraction operations and representation of negative numbers.

The most common types of complements are the 1's complement and 2's complement.

Input A	Input B	Subtract (S) A-B	Borrow (B)
0	0	0	0
0	1	0	1
1	0	1	0
1	1	0	0

Understanding 1's Complement

1's complement is obtained by inverting all bits of a binary number.

It is used to represent negative values, but it has limitations like having two representations for zero.

When adding binary numbers in 1's complement, a carry bit must be added back to the result.

To represent **-34** in 2's complement form

$$+34 = 00100010$$



$$11011101 \quad (\text{1's complement of } +34)$$

$$+ \quad \quad \quad 1$$

$$-34 = 11011110 \quad (\text{2's complement of } +34)$$

Understanding 2's Complement

2's complement is derived by adding 1 to the 1's complement of a binary number.

It provides a unique representation for zero and simplifies binary addition and subtraction.

Most modern computing systems utilize 2's complement for signed binary number representation.

To represent **-34** in 2's complement form

$$+34 = 00100010$$



$$11011101 \quad (\text{1's complement of } +34)$$

$$+ \quad \quad \quad 1$$


$$-34 = 11011110 \quad (\text{2's complement of } +34)$$

Signed Binary Numbers

Signed binary numbers are used to represent both positive and negative integers in binary format.

The leftmost bit, known as the sign bit, indicates the sign of the number (0 for positive, 1 for negative).

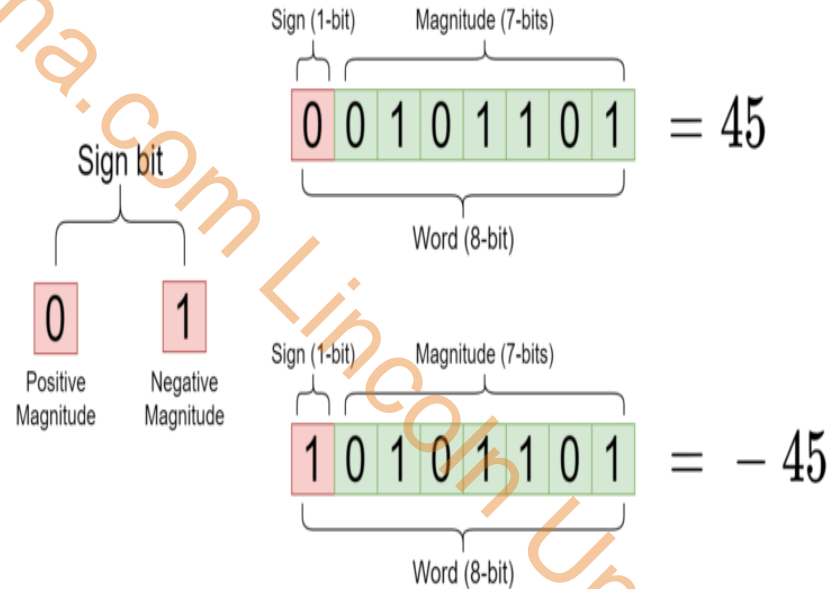Different methods exist for representing signed numbers, with 2's complement being the most widely used.



Binary Codes

Binary codes are systems that represent information in binary form for processing and storage.

Well-known binary codes include ASCII for text representation and Gray code for minimizing errors in digital communication.

Different applications require different coding schemes to optimize performance and reliability.

Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char	Decimal	Hex	Char
0	0	[NULL]	32	20	[SPACE]	64	40	@	96	60	`
1	1	[START OF HEADING]	33	21	!	65	41	A	97	61	a
2	2	[START OF TEXT]	34	22	"	66	42	B	98	62	b
3	3	[END OF TEXT]	35	23	#	67	43	C	99	63	c
4	4	[END OF TRANSMISSION]	36	24	\$	68	44	D	100	64	d
5	5	[ENQUIRY]	37	25	%	69	45	E	101	65	e
6	6	[ACKNOWLEDGE]	38	26	&	70	46	F	102	66	f
7	7	[BELL]	39	27	'	71	47	G	103	67	g
8	8	[BACKSPACE]	40	28	(72	48	H	104	68	h
9	9	[HORIZONTAL TAB]	41	29)	73	49	I	105	69	i
10	A	[LINE FEED]	42	2A	*	74	4A	J	106	6A	j
11	B	[VERTICAL TAB]	43	2B	+	75	4B	K	107	6B	k
12	C	[FORM FEED]	44	2C	,	76	4C	L	108	6C	l
13	D	[CARRIAGE RETURN]	45	2D	-	77	4D	M	109	6D	m
14	E	[SHIFT OUT]	46	2E	.	78	4E	N	110	6E	n
15	F	[SHIFT IN]	47	2F	/	79	4F	O	111	6F	o
16	10	[DATA LINK ESCAPE]	48	30	0	80	50	P	112	70	p
17	11	[DEVICE CONTROL 1]	49	31	1	81	51	Q	113	71	q
18	12	[DEVICE CONTROL 2]	50	32	2	82	52	R	114	72	r
19	13	[DEVICE CONTROL 3]	51	33	3	83	53	S	115	73	s
20	14	[DEVICE CONTROL 4]	52	34	4	84	54	T	116	74	t
21	15	[NEGATIVE ACKNOWLEDGE]	53	35	5	85	55	U	117	75	u
22	16	[SYNCHRONOUS IDLE]	54	36	6	86	56	V	118	76	v
23	17	[ENG OF TRANS. BLOCK]	55	37	7	87	57	W	119	77	w
24	18	[CANCEL]	56	38	8	88	58	X	120	78	x
25	19	[END OF MEDIUM]	57	39	9	89	59	Y	121	79	y
26	1A	[SUBSTITUTE]	58	3A	:	90	5A	Z	122	7A	z
27	1B	[ESCAPE]	59	3B	;	91	5B	[123	7B	{
28	1C	[FILE SEPARATOR]	60	3C	<	92	5C	\	124	7C	
29	1D	[GROUP SEPARATOR]	61	3D	=	93	5D]	125	7D	}
30	1E	[RECORD SEPARATOR]	62	3E	>	94	5E	^	126	7E	~
31	1F	[UNIT SEPARATOR]	63	3F	?	95	5F	_	127	7F	[DEL]

Importance of Binary Storage

Binary storage refers to the method of saving data in a binary format within computing systems.

It is crucial for efficient data retrieval and processing in modern electronic devices.

Various storage devices, such as hard drives and solid-state drives, utilize binary representation for data management.




Registers in Computing

Registers are small, high-speed storage locations within the CPU used to hold temporary data and instructions.

They facilitate quick access to frequently used data, enhancing the overall speed of processing tasks.

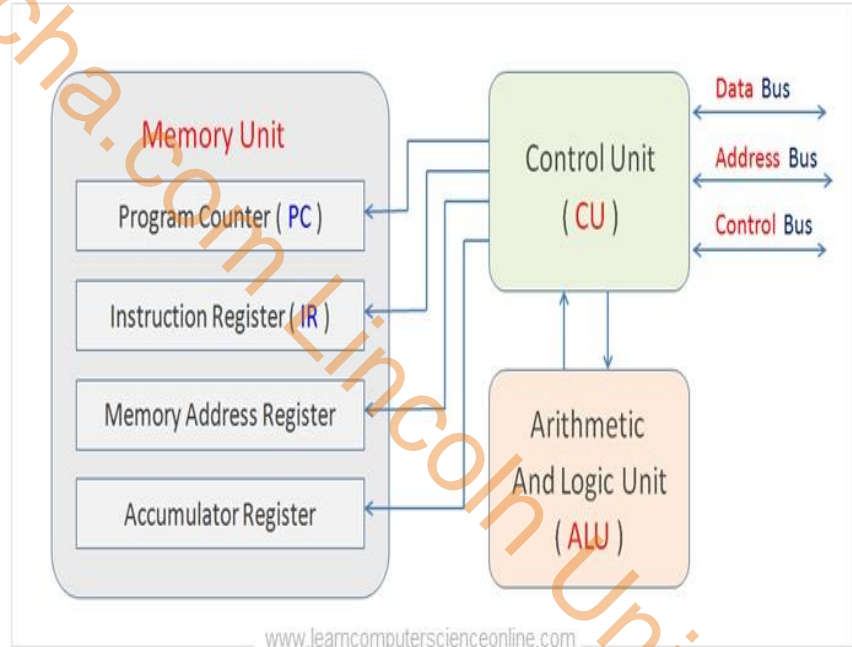Different types of registers exist, including data registers, address registers, and instruction registers.




Memory Hierarchy and Binary Storage

The memory hierarchy in computers organizes storage from fastest to slowest, impacting performance.

Registers, cache, RAM, and secondary storage all play distinct roles in data management.

Understanding this hierarchy is essential for optimizing system performance and resource allocation.

Computer Memory Hierarchy

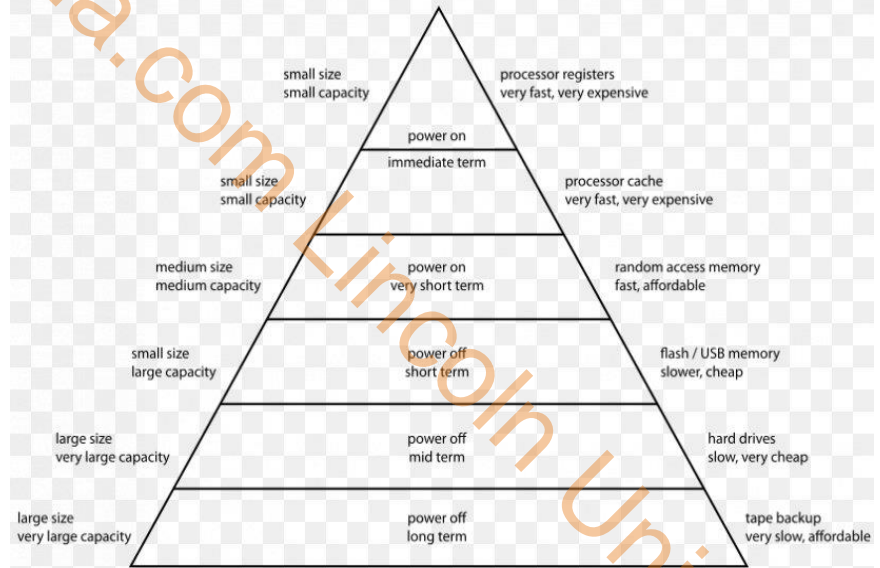

Binary Number Systems in Practice

Binary systems are foundational in digital electronics and computer architecture.

They are used for encoding data, performing arithmetic operations, and executing algorithms.

Proficiency in binary number systems is essential for computer scientists and engineers.

Number Systems

System	Base	Digits
Binary	2	0 1
Octal	8	0 1 2 3 4 5 6 7
Decimal	10	0 1 2 3 4 5 6 7 8 9
Hexadecimal	16	0 1 2 3 4 5 6 7 8 9 A B C D E F

Binary Logic Integrated Circuits


esikhcha.com Lincoln University

Introduction to Binary Logic

Binary logic is the foundation of digital electronics.

It uses two states, typically represented as 0 and 1, to convey information.

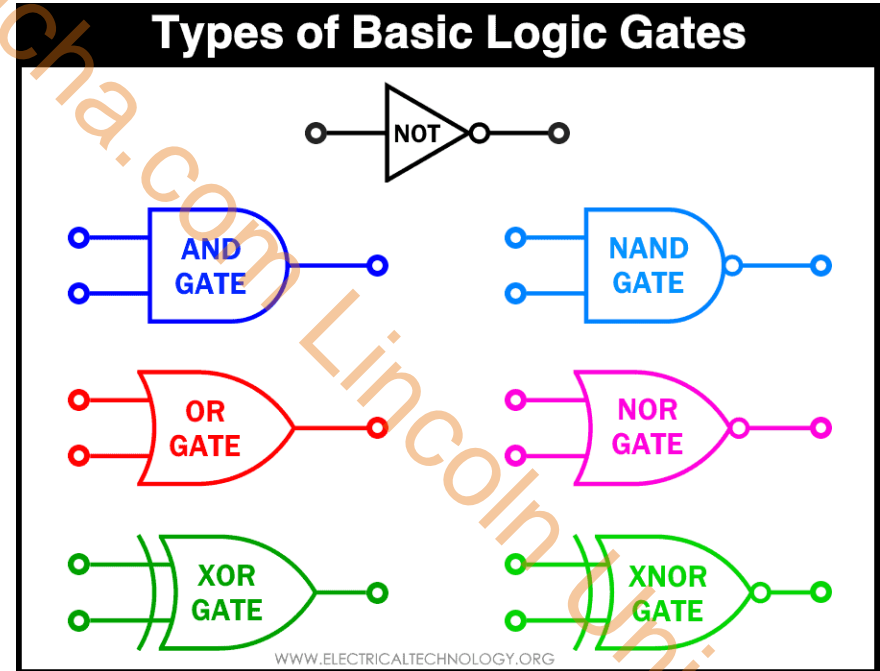The principles of binary logic are essential for the functioning of computers and other digital devices.



Basic Concepts of Binary Logic

Binary digits, or bits, are the smallest unit of data in computing.

Logical operations such as AND, OR, and NOT manipulate these bits to perform computations.

Understanding these operations is crucial for designing efficient digital systems.

Convert the 8 bit binary number 00011010 into denary

128	64	32	16	8	4	2	1
0	0	0	1	1	0	1	0

$$16 + 8 + 2 = 26$$


$$00011010_2 = 26_{10}$$

Truth Tables

A truth table is a mathematical table used to represent the output of logical operations.

Each row of the table corresponds to a unique combination of input values.

 Truth tables help visualize how binary logic functions in different scenarios.




esikhcha.com Lincoln University

Integrated Circuits Overview

Integrated circuits (ICs) are compact assemblies of electronic components.

They are essential for modern electronics, allowing complex circuits to be miniaturized.

 ICs can perform a variety of functions, from simple logic operations to complex processing tasks.



Types of Integrated Circuits

There are two main types of ICs: analog and digital.

Digital ICs are used for binary logic applications, while analog ICs manage continuous signals.

Each type serves specific purposes in electronic devices and systems.



Logic Gates in Integrated Circuits

Logic gates are the fundamental building blocks of digital circuits.

Common logic gates include AND, OR, NOT, NAND, NOR, XOR, and XNOR.


These gates perform binary operations and are implemented within ICs to create complex circuits.

Basic Digital Logic Gates

INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1



AND

 

NAND



OR



NOR




NOT



XOR



XNOR

 

A AND B	$A \cdot B$
A OR B	$A + B$
NOT A	\bar{A}
A XOR B	$A \oplus B$

Applications of Binary Logic and ICs

Binary logic and integrated circuits are used in computers, smartphones, and other digital devices.

They play a crucial role in data processing, storage, and communication technologies.

The integration of logic functions into ICs has revolutionized the field of electronics.



Advantages of Integrated Circuits

ICs offer reduced size and weight compared to discrete components.

They improve reliability and performance due to fewer interconnections.

The mass production of ICs has significantly lowered costs in the electronics industry.



+1-800-295-3800

ALLIED
COMPONENTS
INTERNATIONAL

INTEGRATED CIRCUITS:
TYPES AND
ADVANTAGES OVER
TRADITIONAL
COMPONENTS


 www.alliedcomponents.com

Future Trends in Binary Logic and ICs

Advances in technology are leading to smaller, more powerful integrated circuits.

Emerging fields like quantum computing could redefine binary logic principles.

 Ongoing research aims to create more energy-efficient and versatile ICs for various applications.



Conclusion

Binary logic and integrated circuits are fundamental to modern technology.

Your second bullet

Your third bullet



UNIT 2: BOOLEAN ALGEBRA AND LOGIC GATES

es.inlca.com Lincoln University


**❑ Binary Logic ❑ Switching Circuits And Binary
Signals ❑ Basic Logic Gates: Graphic Symbol**

Introduction to Binary Logic

Binary logic is the foundation of digital computing and electronic systems.

It operates on two discrete values, typically represented as 0 and 1.

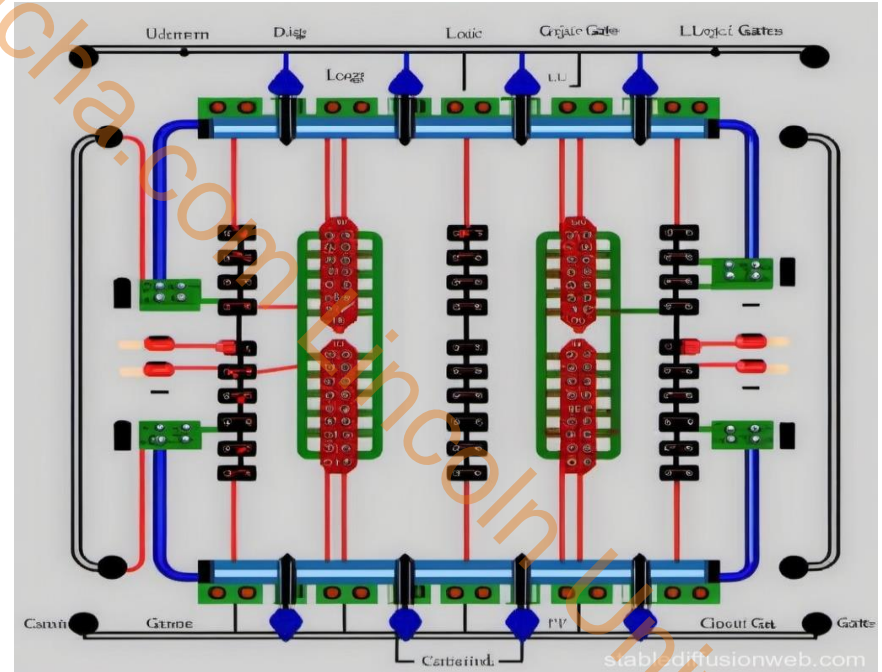Understanding binary logic is crucial for designing and analyzing digital circuits.




Importance of Binary Logic

Binary logic simplifies the representation of complex data and operations.

It serves as a fundamental basis for programming and algorithm development.

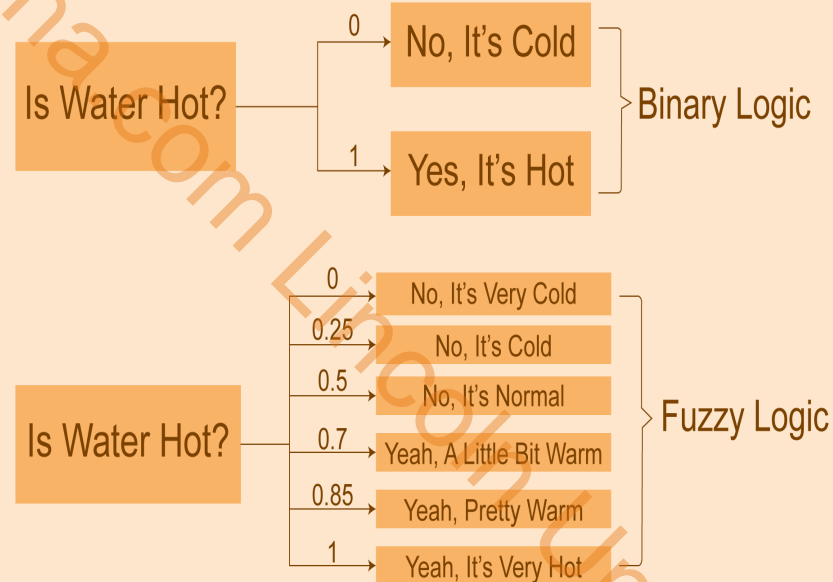Many electronic devices, including computers and smartphones, rely on binary logic.




Overview of Switching Circuits

Switching circuits are used to control the flow of electrical signals in digital systems.

These circuits can switch between different states, typically representing binary values.

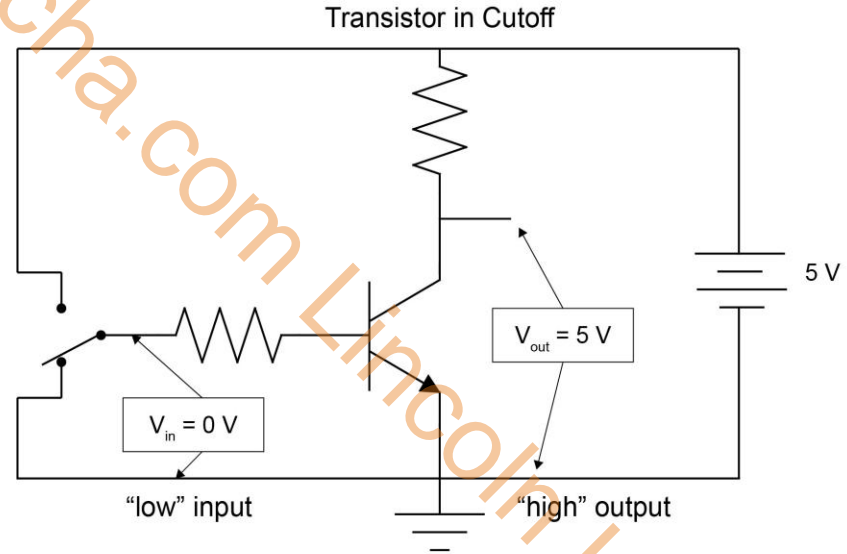They are essential for implementing logic functions and data processing tasks.



0 V = "low" logical level (0)

5 V = "high" logical level (1)

Binary Signals in Switching Circuits

Binary signals are electrical signals that can exist in one of two states: high (1) or low (0).

The representation of binary signals is crucial for reliable data transmission and processing.

Switching circuits interpret these signals to perform logical operations and control functions.

1. Binary signals represent one of two possible states, e.g. 0 or 1, yes or no, current or no current, etc. In electronic systems binary signals can be represented by a voltage on a wire, e.g. 0 V or 3.3 V. Each binary signal carries one "Bit" of information, the unit of information. Answer the questions below:
 - a) How many bits (wires carrying binary signals) are required to represent the output of a motion detector, "motion" or "no motion" detected?
 - b) How many bits are required to represent integers (whole numbers) 0 ... 63?
 - c) How many bits are required to represent integers (whole numbers) 0 ... 100?
 - d) The output voltage of a sensor varies between 0 V and 5 V. How many bits are required to represent that output with a resolution of 1 mV? I.e. the output voltage is rounded to the nearest mV value before representation as a binary signal.

Introduction to Basic Logic Gates

Basic logic gates are the building blocks of digital circuits.

They perform fundamental logical operations such as AND, OR, and NOT.


Logic gates can be combined to create more complex circuits and functions.

Basic Digital Logic Gates

INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1



AND

 

NAND



OR



NOR



NOT



XOR



XNOR



A AND B	$A \cdot B$
A OR B	$A + B$
NOT A	\bar{A}
A XOR B	$A \oplus B$

AND Gate: Graphic Symbol

The AND gate's graphic symbol resembles a D shape with two inputs on the left and one output on the right.

It outputs a high signal (1) only when both inputs are high (1).

This gate is commonly used in various digital applications for decision-making processes.




NOT Gate: Graphic Symbol

The NOT gate, also known as an inverter, has a triangular shape with a small circle at the output.

It inverts the input signal, producing a high signal (1) when the input is low (0), and vice versa.

 This gate is essential for creating complementary signals in digital circuits.




Combining Logic Gates

Logic gates can be combined in various configurations to create complex circuits.

Such combinations allow for the implementation of arithmetic operations and data processing.

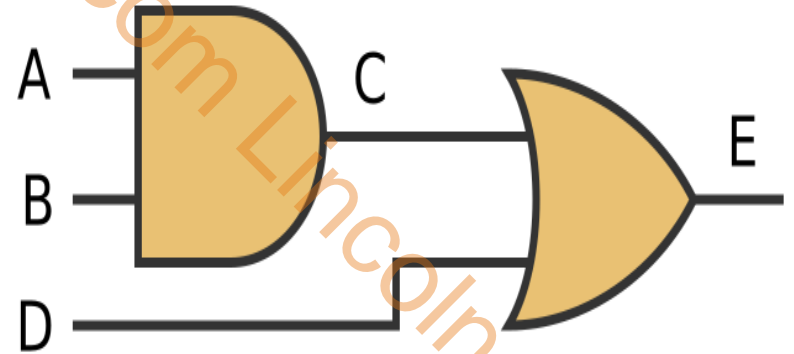Understanding how to manipulate these gates is key to designing effective digital systems.




Conclusion and Applications

Binary logic, switching circuits, and logic gates are integral to modern technology.

Their applications extend to computing, telecommunications, and automation.

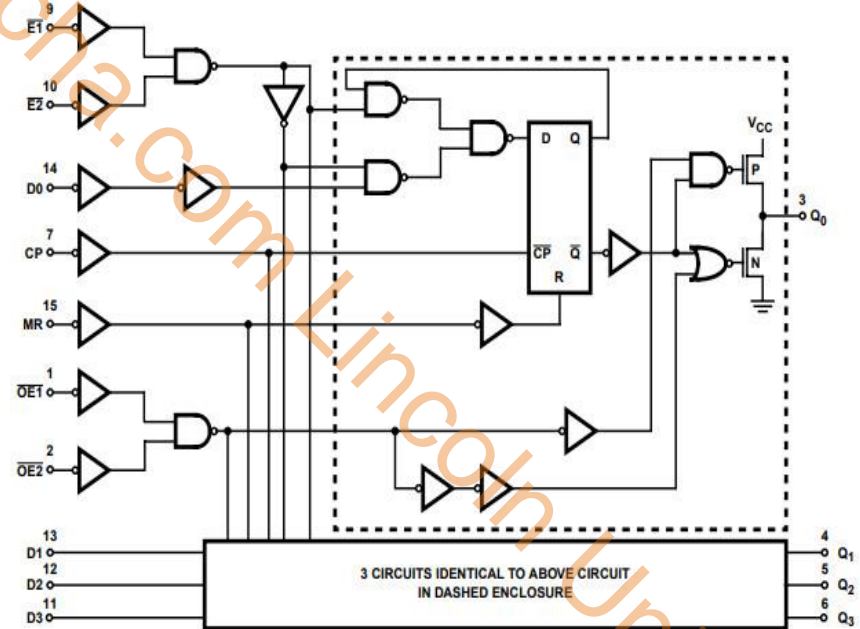A strong grasp of these concepts is essential for anyone pursuing a career in electronics or computer science.



**Timing Diagram: Boolean Algebra: Rule In Boolean
Algebra: Boolean Laws: Commutative
Law: Associative Law**

Introduction to Timing Diagrams

Timing diagrams visually represent the behavior of digital circuits over time.

They show how signals change in response to clock cycles and inputs.

Understanding timing diagrams is crucial for designing reliable electronic systems.



Basics of Boolean Algebra

Boolean algebra is a branch of mathematics that deals with true or false values.

It forms the foundation for digital logic design and circuit simplification.

Boolean expressions use variables and operators like AND, OR, and NOT to represent logic functions.

Laws of Boolean Algebra

Name	AND form	OR form
Identity law	$1.A=A$	$0 + A = A$
Null law	$0.A=0$	$1 + A = 1$
Idempotent law	$A.A=A$	$A + A = A$
Inverse law	$A.\bar{A}=0$	$A + \bar{A} = 1$
Commutative law	$A.B=B.A$	$A + B = B + A$
Associative law	$(AB)C=A(BC)$	$(A+B)+C=A+(B+C)$
Distributive law	$A+BC = (A+B)(A+C)$	$A(B+C)=AB+AC$
Absorption law	$A(A+B) = A$	$A+AB=A$
De Morgan's law	$\overline{A.B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}.\bar{B}$

Importance of Rules in Boolean Algebra

Boolean algebra has specific rules that help simplify complex expressions.

These rules ensure consistent results in logical operations and circuit design.

Mastering these rules is essential for engineers and computer scientists.

Simplify: $A\bar{B} + \overline{(\bar{A} + \bar{B} + C.\bar{C})}$

Solution, $F = A\bar{B} + \overline{(\bar{A} + \bar{B} + C.\bar{C})}$

$$\begin{aligned} &= A\bar{B} + \overline{(\bar{A} + \bar{B} + 0)} \\ &= A\bar{B} + \overline{(\bar{A} + \bar{B})} \\ &= A\bar{B} + (\bar{\bar{A}}.\bar{\bar{B}}) \\ &= A\bar{B} + A.B \\ &= A(\bar{B} + B) \\ &= A.1 \\ &= A \end{aligned}$$

$$A.\bar{A}=0$$

$$A+0=A$$

$$\overline{A + B} = \bar{A}.\bar{B}$$

$$\bar{\bar{A}}=A$$

$$A+\bar{A}=1$$

$$A.1=A$$

Overview of Boolean Laws

Boolean laws include identities, null elements, idempotent laws, and more.

Each law provides a way to manipulate Boolean expressions for simplification.

Familiarity with these laws is necessary for effective circuit design.

Boolean (or Switching) Algebra

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{\bar{A} + \bar{B}} = \bar{A}\bar{B}$


Some identities of Boolean algebra.

The Commutative Law

The commutative law states that the order of variables does not affect the result.

For example, $A + B = B + A$ and A

$B = B$

 


Applications of the Commutative Law

The commutative law can be applied in circuit design to reorder inputs.

It allows for flexibility in logic gate arrangements without altering output.

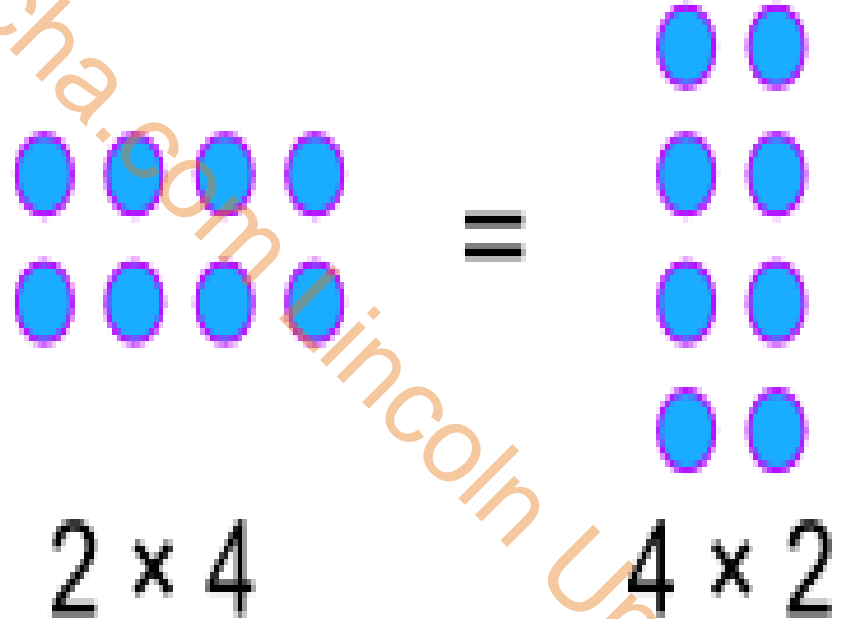Understanding this law aids in optimizing circuit layouts for efficiency.




The Associative Law

The associative law indicates that the grouping of variables does not affect the result.

For instance, $(A + B) + C = A + (B + C)$ and $(A$

Your third bullet

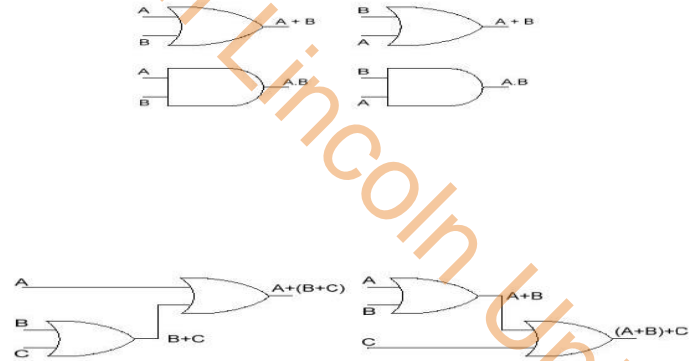


Applications of the Associative Law

The associative law allows for the combination of multiple terms into simpler forms.

It is particularly beneficial in designing circuits with multiple inputs.

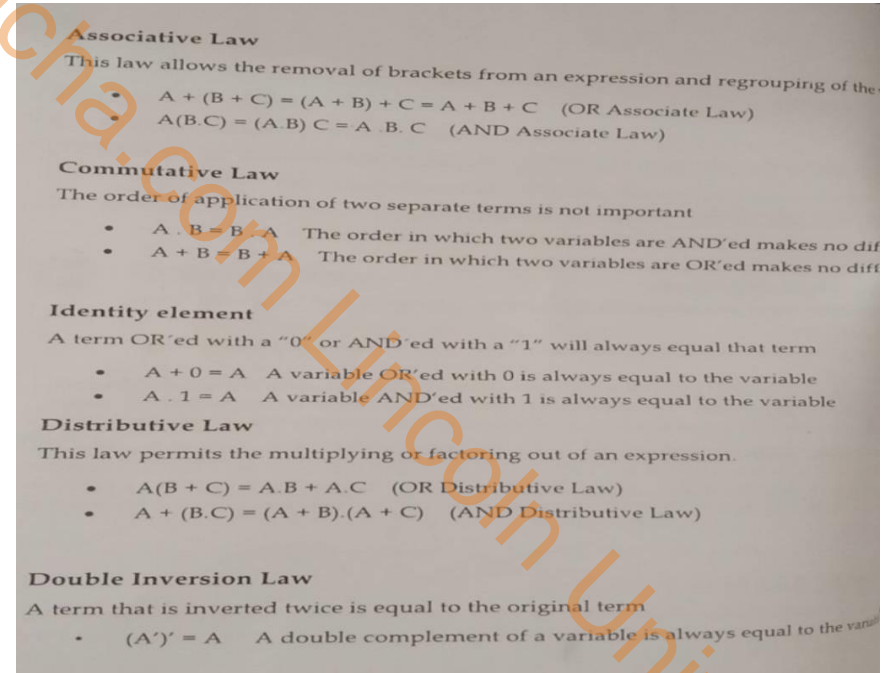Engineers can use this law to streamline logic functions and improve performance.



Combining Commutative and Associative Laws

Both laws can be used together to simplify complex Boolean expressions effectively.

They provide a systematic approach to manipulating logical equations.

Mastery of these laws enhances problem-solving skills in digital logic design.

Law	Description
Commutative law of Addition	$a + b = b + a$
Commutative law of Multiplication	$a \cdot b = b \cdot a$
Associative law of Addition	$a + (b + c) = (a + b) + c$ $a + (b + c) = (a + b) + c$
Associative law of Multiplication	$a \cdot (b \cdot c) = (a \cdot b) \cdot c$ $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
Distributive law	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
Cancellation law of Addition	$a + c = b + c \Leftrightarrow a = b$
Cancellation law of Multiplication	$a \cdot c = b \cdot c \Leftrightarrow a = b$ where $c \neq 0$

**Postulates:Basic Theorems And Properties Of
Boolean Algebra:Operator Precedence:Boolean
Function**


esikhcha.com Lincoln University

Introduction to Boolean Algebra

Boolean Algebra is a mathematical structure that deals with binary variables and logical operations.

Developed by George Boole in the mid-1800s, it serves as the foundation for digital logic design.

 Understanding Boolean algebra is essential for computer science, electronics, and logic circuit design.



oakkhcha.com Lincoln University

Basic Postulates of Boolean Algebra

The basic postulates define the foundational rules that govern Boolean operations.

There are several key postulates, including the identity, null, and complement laws.

These postulates provide the basis for manipulating Boolean expressions and functions.

Basic Rules of Boolean Algebra

1. $A + 0 = A$	7. $A \cdot A = A$
2. $A + 1 = 1$	8. $A \cdot \bar{A} = 0$
3. $A \cdot 0 = 0$	9. $\overline{\overline{A}} = A$
4. $A \cdot 1 = A$	10. $A + AB = A$
5. $A + A = A$	11. $A + \bar{A}B = A + B$
6. $A + \bar{A} = 1$	12. $(A + B)(A + C) = A + BC$

DeMorgan's Theorem

$$\overline{(AB)} = (\bar{A} + \bar{B})$$

$$\overline{(A + B)} = (\bar{A} \bar{B})$$

Fundamental Theorems

Fundamental theorems of Boolean algebra include the idempotent, domination, and double negation theorems.

These theorems help simplify and optimize Boolean expressions for more efficient circuit design.

Each theorem has specific applications, aiding in the transformation of logic circuits.

1.	Law of Identity	$A = A$ $\bar{A} = \bar{A}$
2.	Commutative Law	$A \cdot B = B \cdot A$ $A + B = B + A$
3.	Associative Law	$A \cdot (B \cdot C) = A \cdot B \cdot C$ $A + (B + C) = A + B + C$
4.	Idempotent Law	$A \cdot A = A$ $A + A = A$
5.	Double Negative Law	$\overline{\overline{A}} = A$
6.	Complementary Law	$A \cdot \bar{A} = 0$ $A + \bar{A} = 1$
7.	Law of Intersection	$A \cdot 1 = A$ $A \cdot 0 = 0$
8.	Law of Union	$A + 1 = 1$ $A + 0 = A$
9.	DeMorgan's Theorem	$\overline{AB} = \bar{A} + \bar{B}$ $\overline{A + B} = \bar{A} \bar{B}$
10.	Distributive Law	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ $A + (BC) = (A + B) \cdot (A + C)$
11.	Law of Absorption	$A \cdot (A + B) = A$ $A + (AB) = A$
12.	Law of Common Identities	$A \cdot (\bar{A} + B) = AB$ $A + (\bar{A}B) = A + B$

Properties of Boolean Algebra

Boolean algebra has several important properties, such as commutativity, associativity, and distributivity.

These properties allow for the rearrangement and simplification of logical expressions.

Understanding these properties is crucial for both theoretical and practical applications in computer engineering.

Laws of Boolean Algebra


Name	AND form	OR form
Identity law	$1.A=A$	$0 + A = A$
Null law	$0.A=0$	$1 + A = 1$
Idempotent law	$A.A=A$	$A + A = A$
Inverse law	$A.\bar{A}=0$	$A + \bar{A} = 1$
Commutative law	$A.B=B.A$	$A + B = B + A$
Associative law	$(AB)C=A(BC)$	$(A+B)+C=A+(B+C)$
Distributive law	$A+BC = (A+B)(A+C)$	$A(B+C)=AB+AC$
Absorption law	$A(A+B) = A$	$A+AB=A$
De Morgan's law	$\overline{A.B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}.\bar{B}$

Operator Precedence in Boolean Algebra

Operator precedence determines the order in which operations are performed in Boolean expressions.

The standard precedence follows a specific hierarchy, similar to arithmetic operations.

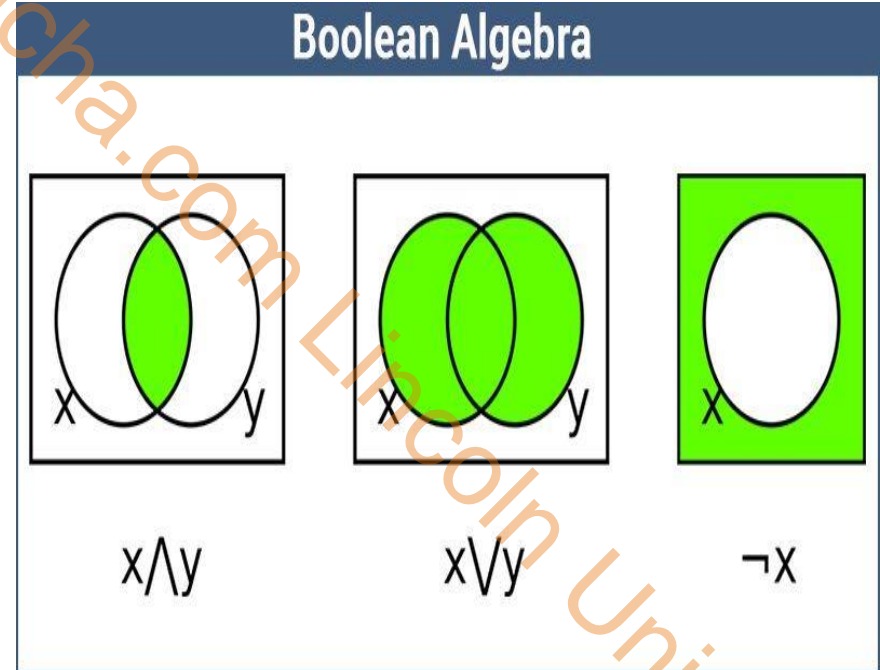Knowing operator precedence is essential for correctly interpreting and simplifying Boolean expressions.



The AND Operator

The AND operator is represented by the multiplication symbol (\cdot) or simply by juxtaposition.

It returns true only when both operands are true, embodying the concept of logical conjunction.

The AND operator is fundamental in constructing complex logical functions and circuits.

esikhcha.com Lincoln University

The OR Operator

The OR operator is represented by the addition symbol (+) in Boolean algebra.

It returns true if at least one of the operands is true, representing logical disjunction.

This operator is widely used in decision-making processes and circuit designs.




The NOT Operator

The NOT operator is a unary operator that inverts the value of a Boolean variable.

It is commonly represented by an overline or the symbol (\neg).

 Understanding the NOT operator is essential for creating complementary logic and circuits.



Boolean Functions

A Boolean function is a mapping from a set of binary inputs to a single binary output.

These functions can be expressed in various forms, including truth tables, algebraic expressions, and logic diagrams.

Boolean functions are crucial for designing and analyzing digital circuits and systems.

Function	x	0	0	1	1
	y	0	1	0	1
Constant 0	0	0	0	0	0
And	$x \cdot y$	0	0	0	1
x And Not y	$x \cdot \bar{y}$	0	0	1	0
x	x	0	0	1	1
Not x And y	$\bar{x} \cdot y$	0	1	0	0
y	y	0	1	0	1
Xor	$x \cdot \bar{y} + \bar{x} \cdot y$	0	1	1	0
Or	$x + y$	0	1	1	1
Nor	$\overline{x + y}$	1	0	0	0
Equivalence	$x \cdot y + \bar{x} \cdot \bar{y}$	1	0	0	1
Not y	\bar{y}	1	0	1	0
If y then x	$x + \bar{y}$	1	0	1	1
Not x	\bar{x}	1	1	0	0
If x then y	$\bar{x} + y$	1	1	0	1
Nand	$\overline{x \cdot y}$	1	1	1	0
Constant 1	1	1	1	1	1

Applications of Boolean Algebra

Boolean algebra has numerous applications in computer science, particularly in digital circuit design.

It is used in programming, database design, and artificial intelligence for logical reasoning.

Mastery of Boolean algebra enables efficient problem-solving and optimization in technology.

Simplify: $A\bar{B} + \overline{(\bar{A} + \bar{B} + C.\bar{C})}$

Solution, $F = A\bar{B} + \overline{(\bar{A} + \bar{B} + C.\bar{C})}$

$$\begin{aligned} &= A\bar{B} + \overline{(\bar{A} + \bar{B} + 0)} \\ &= A\bar{B} + \overline{(\bar{A} + \bar{B})} \\ &= A\bar{B} + (\bar{\bar{A}}.\bar{\bar{B}}) \\ &= A\bar{B} + A.B \\ &= A(\bar{B} + B) \\ &= A.1 \\ &= A \end{aligned}$$

$$A.\bar{A}=0$$

$$A+0=A$$

$$\overline{A + B} = \bar{A}.\bar{B}$$

$$\bar{\bar{A}}=A$$

$$A+\bar{A}=1$$

$$A.1=A$$

UNIT 3:
SIMPLIFICATION OF
BOOLEAN FUNCTION

esikhcha.com Lincoln University

**Universal Gates □ IC Digital Logic Families □
Propagation Delay**


esikhcha.com Lincoln University

Introduction to Universal Gates

Universal gates are fundamental components in digital logic design, capable of implementing any Boolean function.

The most common universal gates are NAND and NOR gates, which can be used to construct all other basic gates.

 Understanding universal gates is essential for simplifying digital circuits and enhancing their functionality.




Characteristics of Universal Gates

Universal gates can create any logic circuit using just one type of gate, simplifying design and manufacturing.

They provide versatility, as they can be combined in various configurations to achieve desired outputs.

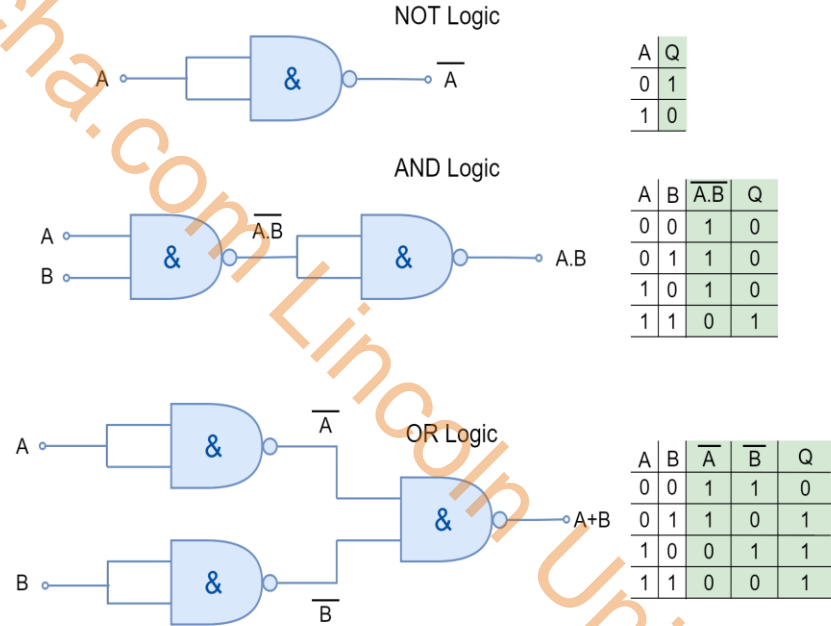The ability to implement any Boolean expression makes universal gates crucial in digital electronics.




IC Digital Logic Families Overview

Integrated Circuit (IC) digital logic families are groups of related logic gates that share similar characteristics and performance.

Common families include TTL (Transistor-Transistor Logic), CMOS (Complementary Metal-Oxide-Semiconductor), and ECL (Emitter-Coupled Logic).

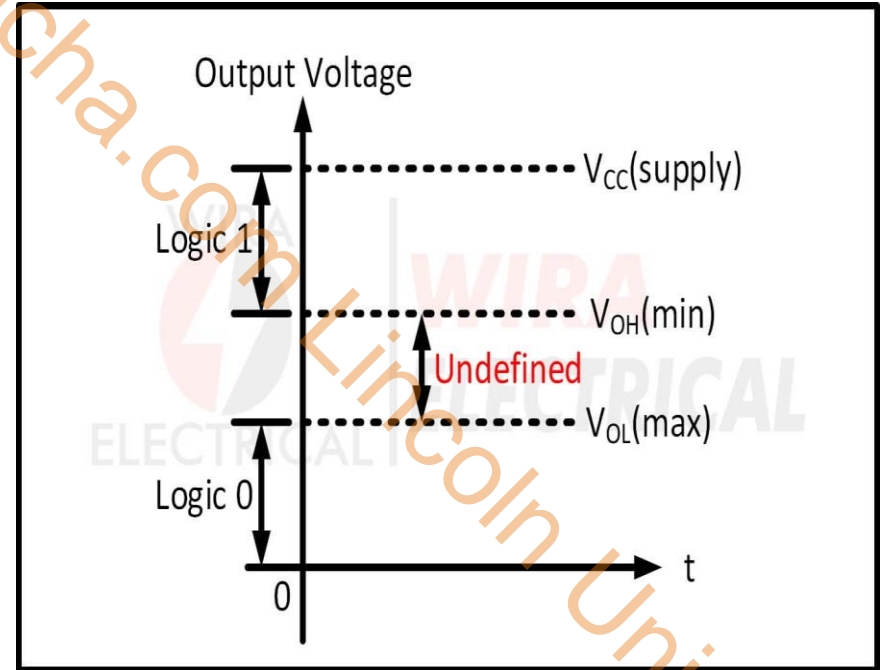Each family has specific applications, power consumption levels, and speed, influencing their selection for various projects.



TTL Logic Family

TTL is one of the earliest and most widely used logic families, characterized by its fast switching times and moderate power consumption.

It operates with a standard voltage range of 4.75V to 5.25V, making it compatible with many digital circuits.

TTL devices are known for their robustness and ease of use, though they can be less power-efficient compared to newer families.

TTL and CMOS logic levels

- ♦ TTL ≡ Transistor-transistor logic (bipolar transistors)
- ♦ CMOS ≡ Complementary metal oxide semiconductor
- ♦ TTL I/O are closer to ground than CMOS
 - ◊ Logic families not 100% compatible
 - ◊ More about this later

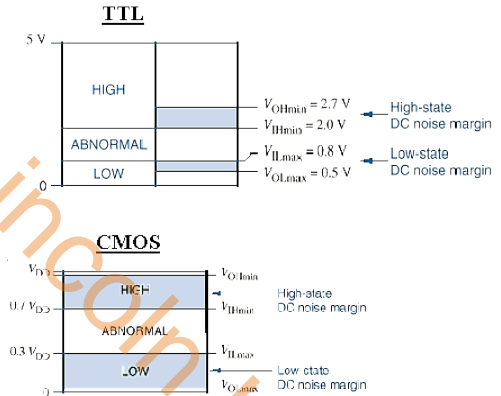



Figure 3-26 Logic levels and noise margins for the HC-series CMOS logic family.

CMOS Logic Family

CMOS technology is known for its low power consumption and high noise immunity, making it ideal for battery-operated devices.

This family operates on a wider voltage range and can achieve higher densities of logic functions on a single chip.

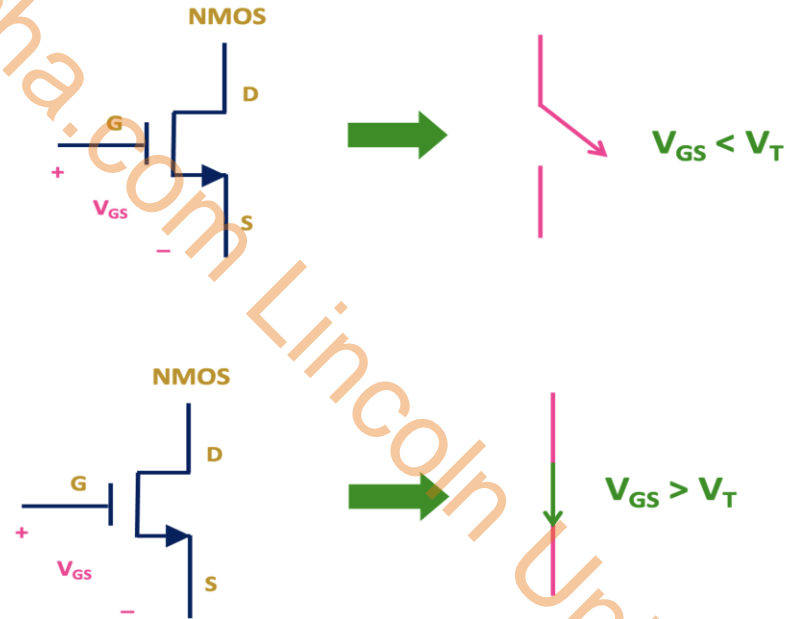CMOS gates switch slower than TTL but offer better performance in high-speed applications due to their lower heat generation.




ECL Logic Family

Emitter-Coupled Logic (ECL) is known for its very high speed, making it suitable for high-frequency applications like telecommunications.

ECL devices operate at a higher voltage range, typically from -5.2V to -4.5V, which can complicate circuit design.

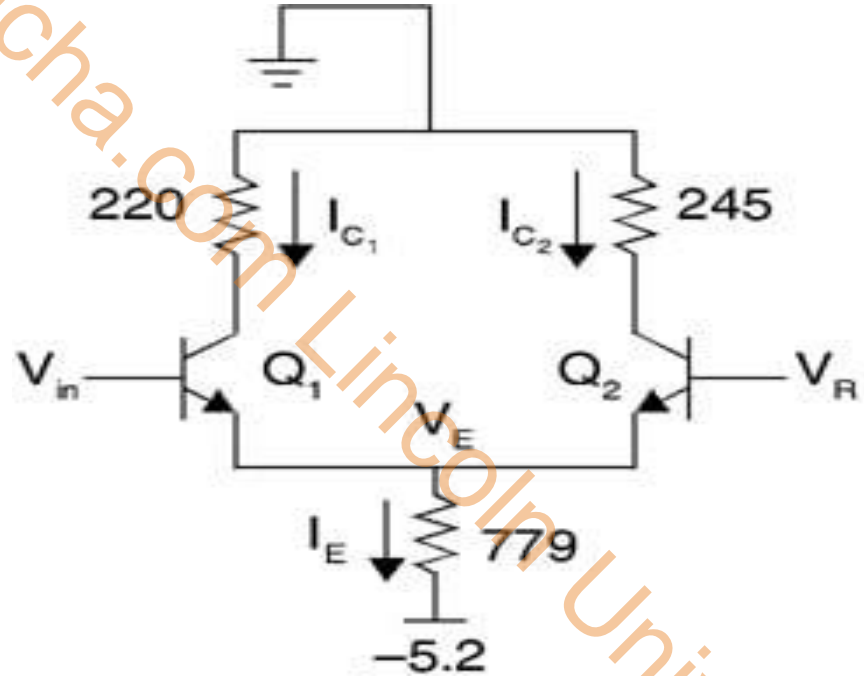While ECL provides superior speed, it also comes with higher power consumption and cost compared to other families.



Propagation Delay Explained

Propagation delay is the time it takes for a signal to travel through a logic gate, affecting overall circuit performance.

It is a critical parameter in digital design, as it influences the maximum operating frequency of a circuit.

Understanding propagation delay helps engineers optimize circuit designs for speed and efficiency.




esikhcha.com Lincoln University

Factors Affecting Propagation Delay

Several factors can influence propagation delay, including temperature, supply voltage, and load capacitance.

The type of logic family also plays a significant role, with different families exhibiting varying propagation delays.

 Designers often need to balance propagation delay with power consumption and circuit complexity in their designs.




Measuring Propagation Delay

Propagation delay is typically measured using time-domain reflectometry or oscilloscopes to analyze signal transitions.

It is essential to measure both the rising and falling edges of the signal to get an accurate representation of delay.

 Understanding how to measure and analyze propagation delay is critical for successful digital circuit design.




Conclusion and Applications

Universal gates, IC digital logic families, and propagation delay are essential concepts in digital electronics.

Mastering these topics enables engineers to design efficient, reliable, and high-performance digital circuits.

 Their applications range from simple consumer electronics to complex computer systems, underscoring their importance in modern technology.



SOP And POS \Rightarrow K-Map Details

esikhcha.com Lincoln University

Introduction to SOP and POS

SOP and POS are two fundamental forms of representing Boolean functions.

They are essential for simplifying logic expressions in digital circuit design.

Understanding these forms is crucial for optimizing circuit performance.

Representation of Boolean Expression

Boolean expressions can be represented in 2 forms

1. Sum of product - SOP
2. Product of sum - POS

SOP Eg: $AB+BC, \bar{A}\bar{B} + \bar{A}\bar{B}$

POS Eg: $(A+B).(B+C)$

These expressions are in SOP & POS forms but they are not in standard SOP & POS.

They are not unique.

$$A\bar{B} + B\bar{C} \rightarrow \uparrow \text{ literals } A, \bar{A}, B, C$$

$$\dots \bar{A}\bar{B} + B\bar{C}(A+\bar{A})$$

$$= \bar{A}\bar{B} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} \rightarrow A, \bar{B}, \bar{A}, B, \bar{C}, \bar{A}\bar{B}, \bar{C}$$

The variables and its complements are referred to as literals.

Definition of SOP

The Sum of Products (SOP) is a canonical form for Boolean expressions.

It consists of multiple product terms summed together.

Each product term represents a set of conditions under which the function outputs true.

		ab			
		00	01	11	10
cd	00	0	1	1	1
	01	0	1	1	0
	11	0	1	0	0
	10	1	0	0	1

$$g = \sum m(2,4,5,7,8,10,12,13)$$


$$g = \prod M(0,1,3,6,9,11,14,15)$$

Definition of POS

Product of Sums (POS) is another canonical form for Boolean expressions.

It is composed of multiple sum terms multiplied together.

 Each sum term represents a set of conditions under which the function outputs false.



Conversion from Truth Table to SOP

To convert a truth table to SOP, identify all rows where the output is true.

Each true output row contributes a product term to the SOP expression.

Combine all product terms using the OR operator to form the final SOP.

Convert the following SOP expressions to POS form:

$$F(A,B,C) = ABC + AB'C' + AB'C + ABC' + A'B'C$$

111 100 101 110 001

$$= \sum m(1,4,5,6,7)$$

$$= \prod M(0,2,3)$$

$$0_{10} = 000_2 \quad 2_{10} = 010_2 \quad 3_{10} = 011_2$$

A+B+C A+B'+C A+B'+C'

$$F(A,B,C) = (A + B + C)(A + B' + C)(A + B' + C')$$

<u>SOP</u>
A = 1
A' = 0

<u>POS</u>
A = 0
A' = 1



K-Map Overview

A Karnaugh Map (K-Map) is a visual tool used to simplify Boolean expressions.

It provides a systematic way to group adjacent cells representing minterms or maxterms.

K-Maps help to minimize SOP and POS forms effectively.

A Karnaugh map (K-Map) is a visual method used to simplify the algebraic expressions in Boolean functions without having to use, remember or manipulate each and every Boolean algebraic theorem. It involves fewer steps than the Boolean algebraic minimization technique to arrive at a simplified expression.

- (a) Simplify the following Boolean expression of output X using K-Map:

$$X = \bar{A}\bar{B}\bar{D} + BCD + \bar{A}B\bar{C}D + CD \quad (10 \text{ marks})$$

- (b) Design the logic control circuit of **Figure 3**. The control circuit functions to turn **ON** the light bulb whenever the binary inputs are even numbers between 1 and 15 in decimal. Other than that, the light bulb turns **OFF**. In your design, include:

- the truth table deduced from the description. (8 marks)
- the simplified output expression using K-Map. (5 marks)
- the logic control circuit using combinational logic gates. (2 marks)

 


Figure 3

SOP Simplification using K-Map

In a K-Map, mark the cells corresponding to the minterms of the SOP expression.

Group the marked cells into rectangles, each representing a product term.

The resulting simplified expression is derived from the groups formed.

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	1	1	0
10	1	0	0	0

POS Simplification using K-Map


For POS simplification, mark the cells corresponding to the maxterms of the function.

Group the unmarked cells in rectangles, each representing a sum term.

The final POS expression is obtained from these groups.

K-map Simplification of POS Expression
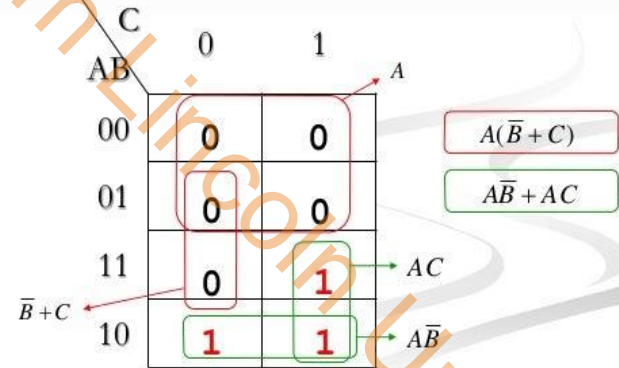
$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)$$




Advantages of K-Maps

K-Maps simplify the process of minimizing Boolean expressions visually.

They reduce the likelihood of errors compared to algebraic simplification methods.

 K-Maps are particularly useful for functions with up to six variables.



esikhcha.com Lincoln University

Conclusion

Understanding SOP, POS, and K-Maps is essential for digital circuit design.

These tools enhance the ability to create efficient and effective logical circuits.

Mastery of these concepts is beneficial for students and professionals in electronics.

SOP and POS Examples

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$Y(A,B,C) = \sum m(0,2,3,6,7)$

1,4,5

$Y(A,B,C) = \prod M(1,4,5)$

$Y = \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$

Canonical SOP form

16 / Digital Electronics

NAND And NOR Implementation ☐ Canonical And Standard Forms ☐ Truth Tables


esikhcha.com Lincoln University

Introduction to NAND and NOR Gates

NAND and NOR gates are fundamental building blocks in digital electronics.

Both gates are universal, meaning they can be used to create any digital logic circuit.

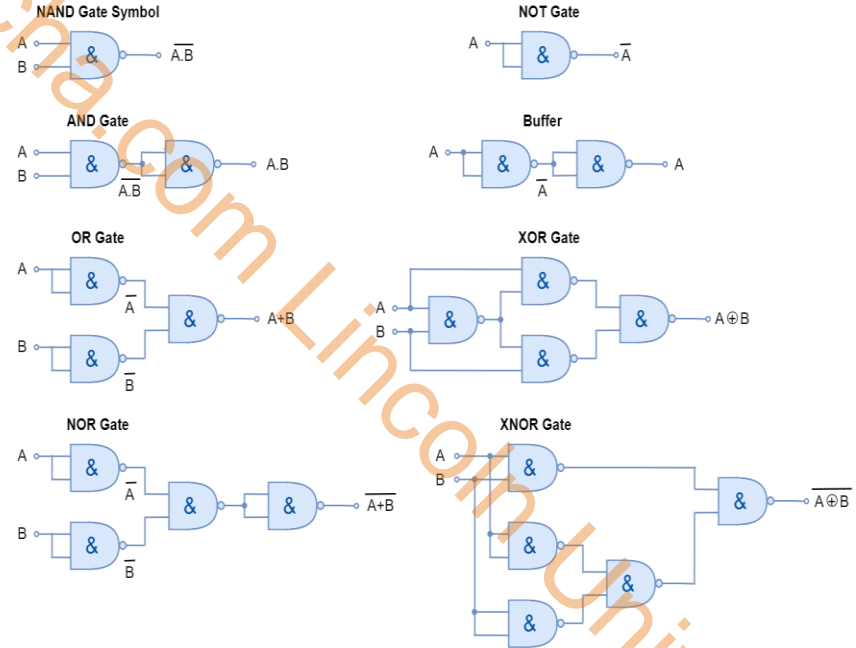Their implementations are crucial in simplifying complex logical expressions.




Characteristics of NAND Gates

A NAND gate produces a low output only when all its inputs are high.

The truth table for a NAND gate shows that the output is the inverse of an AND gate.

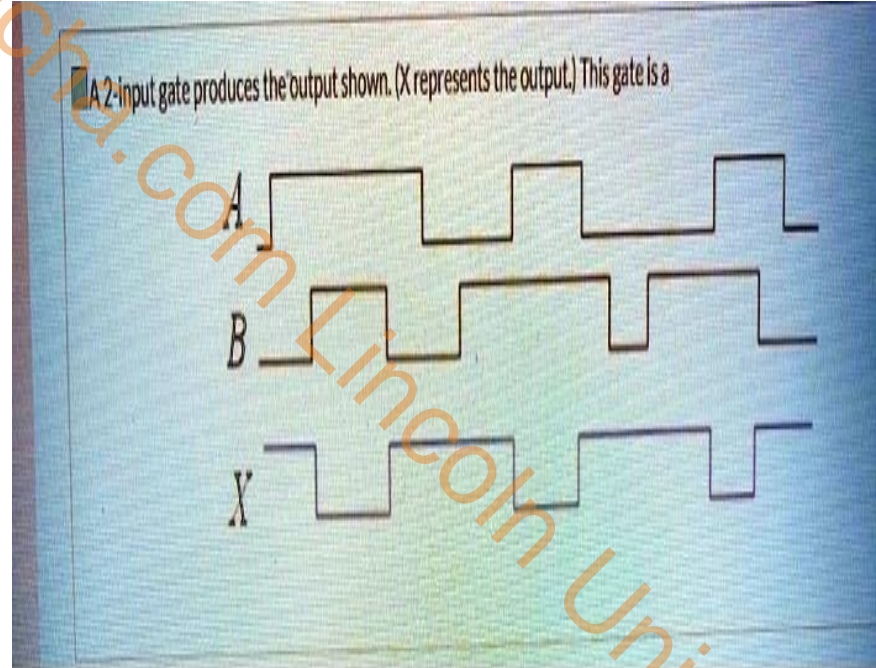It is widely used in various applications due to its versatility and ease of use.




Characteristics of NOR Gates

A NOR gate produces a high output only when all its inputs are low.

The truth table for a NOR gate indicates that the output is the inverse of an OR gate.

 Like NAND gates, NOR gates can also be employed to create any other logical function.




Truth Tables for NAND Gates

The truth table for a 2-input NAND gate consists of four possible input combinations.

The output of the NAND gate is high for three combinations and low for one.

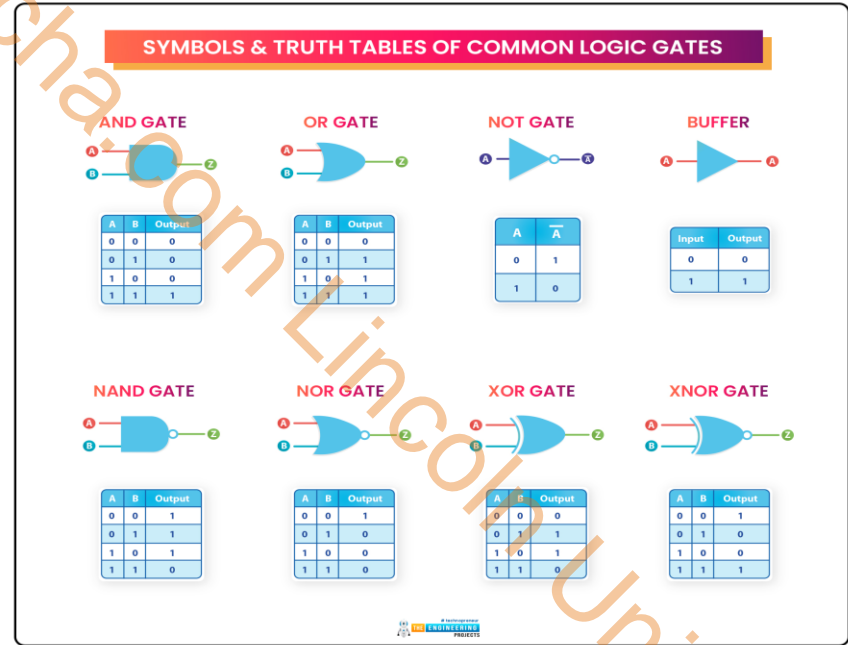Understanding the truth table is essential for designing circuits using NAND gates.




Truth Tables for NOR Gates

The truth table for a 2-input NOR gate also consists of four possible input combinations.

The output of the NOR gate is high for only one combination and low for the others.

 This truth table is crucial for implementing logic circuits with NOR gates.



Truth Table of 3-input XNOR Gate			
A	B	C	Q
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Canonical Forms Overview

Canonical forms are standardized ways of representing logical expressions.

They include Sum of Products (SOP) and Product of Sums (POS) forms.

These forms are essential for simplifying and implementing digital circuits.

Lecture on 3-25 SA305 Spring 2013

1 Canonical Form

To construct the simplex method we need to put our linear programs all in a similar form so that the algorithm is standardized and can use the mechanics of the extreme points.

Definition 1.1. A linear program with n variables is in *canonical form* if it is of the following form:

$$\begin{aligned} \max \quad & c^T x \\ \text{subject to} \quad & Ax = b \\ & x \geq 0 \end{aligned}$$

where $A = (a_{ij})$ is a $m \times n$ matrix, $m \leq n$, and the rows of A are linearly independent.

Can every linear program be put in canonical form? First let's look at an example.

Example 1.2. Let

$$\begin{aligned} x + 2y &\leq 1 \\ 2x + y &\geq 1 \\ x, y &\geq 0 \end{aligned}$$

be the constraints of a LP.

For each constraint where there might be **slack** or **surplus** you add or subtract a slack or surplus variable to make the constraint equality and then append the LP with the non-negativity of these new variables.

So our new constraints look like

$$\begin{aligned} x + 2y + s_1 &= 1 \\ 2x + y - s_2 &= 1 \\ x, y, s_1, s_2 &\geq 0. \end{aligned}$$

Now let's put this in matrix

$$A = \begin{bmatrix} 1 & 2 & 1 & 0 \\ 2 & 1 & 0 & -1 \end{bmatrix}$$


and

Canonical Sum of Products (SOP)

The SOP form is created by summing the products of the input variables.

Each product term corresponds to a row in the truth table where the output is high.

 This form can be implemented using NAND gates by applying De Morgan's theorem.




Canonical Product of Sums (POS)

The POS form is generated by multiplying the sums of the input variables.

Each sum term corresponds to a row in the truth table where the output is low.

 NOR gates can be used to implement the POS form effectively.



Standard Forms and Their Importance

Standard forms are simplified versions of canonical forms for ease of implementation.

They reduce the complexity of logical expressions, making circuit design more efficient.

Understanding standard forms helps in optimizing digital circuits for performance and cost.

Lecture on 3-25 SA305 Spring 2013

1 Canonical Form

To construct the simplex method we need to put our linear programs all in a similar form so that the algorithm is standardized and can use the mechanics of the extreme points.

Definition 1.1. A linear program with n variables is in *canonical form* if it is of the following form:

$$\begin{aligned} \max \quad & c^T x \\ A x &= b \\ x &\geq 0 \end{aligned}$$

where $A = (a_{ij})$ is a $m \times n$ matrix, $m \leq n$, and the rows of A are linearly independent.

Can every linear program be put in canonical form? First let's look at an example.

Example 1.2. Let

$$\begin{aligned} x + 2y &\leq 1 \\ 2x + y &\geq 1 \\ x, y &\geq 0 \end{aligned}$$

be the constraints of a LP.

For each constraint where there might be **slack** or **surplus** you add or subtract a slack or surplus variable to **make** the constraint equality and then append the LP with the non-negativity of these new variables.

So our new constraints look like

$$\begin{aligned} x + 2y + s_1 &= 1 \\ 2x + y - s_2 &= 1 \\ x, y, s_1, s_2 &\geq 0. \end{aligned}$$

Now let's put this in matrix

$$A = \begin{bmatrix} 1 & 2 & 1 & 0 \\ 2 & 1 & 0 & -1 \end{bmatrix}$$


and

Conclusion and Applications

NAND and NOR gates are essential in creating efficient digital systems.

Mastery of truth tables and canonical forms is vital for anyone in electronics or computer engineering.

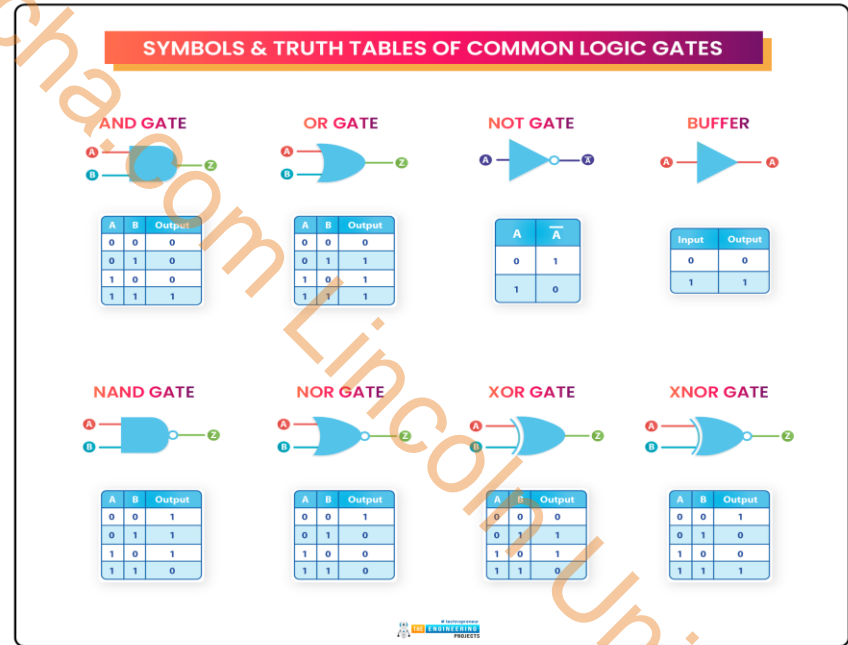Their applications range from simple circuits to complex computational systems in modern technology.



Two – Variable Map \square **Three – Variable Map** \square **Four – Variable Map**

esikhcha.com Lincoln University

Introduction to Variable Maps

Variable maps are a visual representation used in Boolean algebra and digital logic design.

They help simplify complex logical expressions by organizing truth values systematically.

Understanding two, three, and four-variable maps is essential for designing efficient digital circuits.

What is Boolean Algebra?

Basic Rules of Boolean Algebra

1. $A + 0 = A$	7. $A \cdot A = A$
2. $A + 1 = 1$	8. $A \cdot \bar{A} = 0$
3. $A \cdot 0 = 0$	9. $\bar{\bar{A}} = A$
4. $A \cdot 1 = A$	10. $A + AB = A$
5. $A + A = A$	11. $A + \bar{A}B = A + B$
6. $A + \bar{A} = 1$	12. $(A + B)(A + C) = A + BC$


DeMorgan's Theorem

$$\overline{(AB)} = \bar{A} + \bar{B}$$

$$\overline{(A + B)} = \bar{A} \bar{B}$$

Commutative Property of Addition

$$A + B = B + A$$

 


Electrical 4 U

Two-Variable Map Overview

A two-variable map is a grid that represents all possible combinations of two input variables.

The map consists of four cells, each corresponding to a unique combination of the variables' truth values.

 It is commonly used to simplify Boolean expressions involving two variables using grouping methods.




Creating a Two-Variable Map

To create a two-variable map, list the variables along the rows and columns of a 2x2 grid.

Fill in the cells based on the output values of the logical expression for each input combination.

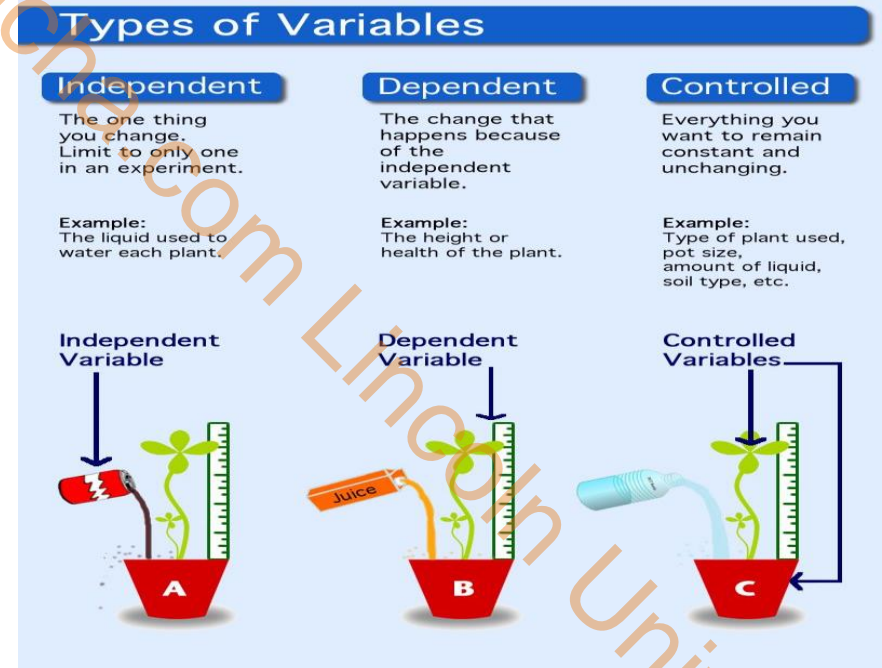Group adjacent cells with '1's to identify simplified product terms in the expression.




Example of a Two-Variable Map

Consider the expression $F(A, B) = AB + A'B$.

The corresponding two-variable map will have '1's in the appropriate cells based on the truth table.

This visual representation makes it easier to identify simplifications and redundancies.

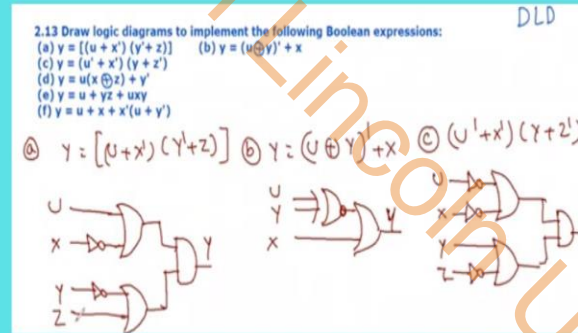2.13 Draw logic diagrams to implement the following Boolean expressions: (a) $y = [(u + x')(y' + z)]$ (b) $y = (u' y)' + x$ (c) $y = (u' + x')(y + z)'$ (d) $y = u(x'z) + y'$ (e) $y = u + yz + uxy$ (f) $y = u + x + x'(u + y')$



B.Tech
GATE
IES

Three-Variable Map Overview

A three-variable map expands the concept to include three input variables, resulting in an 8-cell grid.

Each cell represents a unique combination of the variables' truth values, allowing for more complex expressions.

This map is particularly useful for simplifying Boolean functions involving three variables.

ab c	00	01	11	10
0	000 (0)	010 (2)	110 (6)	100 (4)
1	001 (1)	011 (3)	111 (7)	101 (5)


Fig. 2.18 The three-variable K-map

Creating a Three-Variable Map

To create a three-variable map, organize the variables in a 2x4 grid format.

Fill the cells according to the output values derived from the logical expression for each combination.

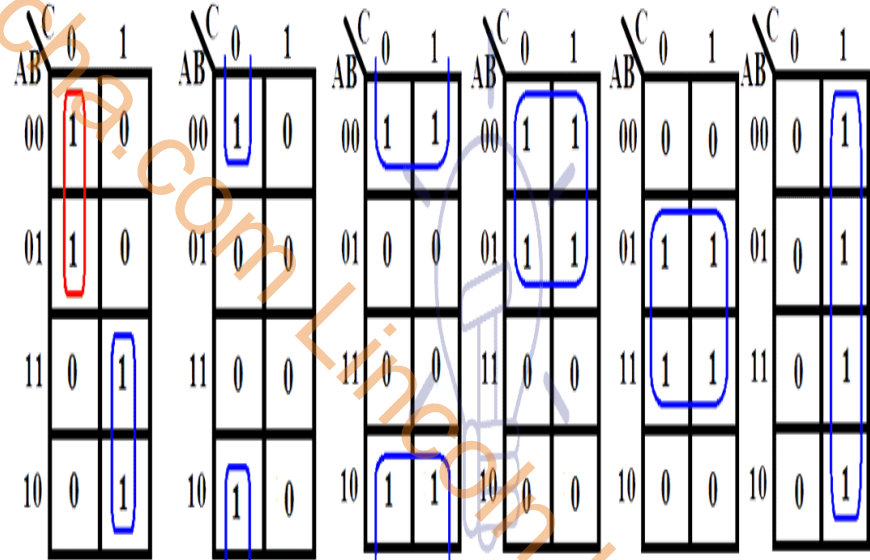Groups of adjacent '1's can be combined to simplify the Boolean function efficiently.



Groups of 2

www.electricaltechnology.org

Groups of 4

Example of a Three-Variable Map

For the expression $F(A, B, C) = ABC + AB'C + A'BC'$, we can create a corresponding three-variable map.

Each cell is filled based on the truth table values for the expression.

This helps visualize potential simplifications and optimal circuit designs.

$$\text{Given: } X = \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}cD + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BcD + \bar{A}B\bar{C}\bar{D} + AB\bar{C}\bar{D} + ABc\bar{D} + AB\bar{C}D + ABcD + A\bar{B}C\bar{D} + A\bar{B}cD + A\bar{B}C\bar{D} + A\bar{B}cD$$


		CD			
		00	01	11	10
AB	00	0 1	1 0	3 1	2 1
	01	4 1	5 0	7 1	6 1
	11	12 1	13 0	15 1	14 1
	10	8 0	9 0	11 0	10 0

Four-Variable Map Overview

A four-variable map introduces even more complexity, represented by a 16-cell grid.

Each cell corresponds to a unique combination of four input variables, allowing for comprehensive analysis.

 This map is ideal for simplifying Boolean expressions with four variables, streamlining circuit design.




Creating a Four-Variable Map

To create a four-variable map, arrange the variables in a 4x4 grid format for clarity.

The cells are filled similarly to the previous variable maps, reflecting the output of the logical expression.

 Identifying groups of adjacent '1's aids in the simplification process for the expression.




Conclusion and Applications

Two, three, and four-variable maps are essential tools in digital logic design and simplification.

These maps facilitate the understanding of complex Boolean expressions and enhance circuit efficiency.

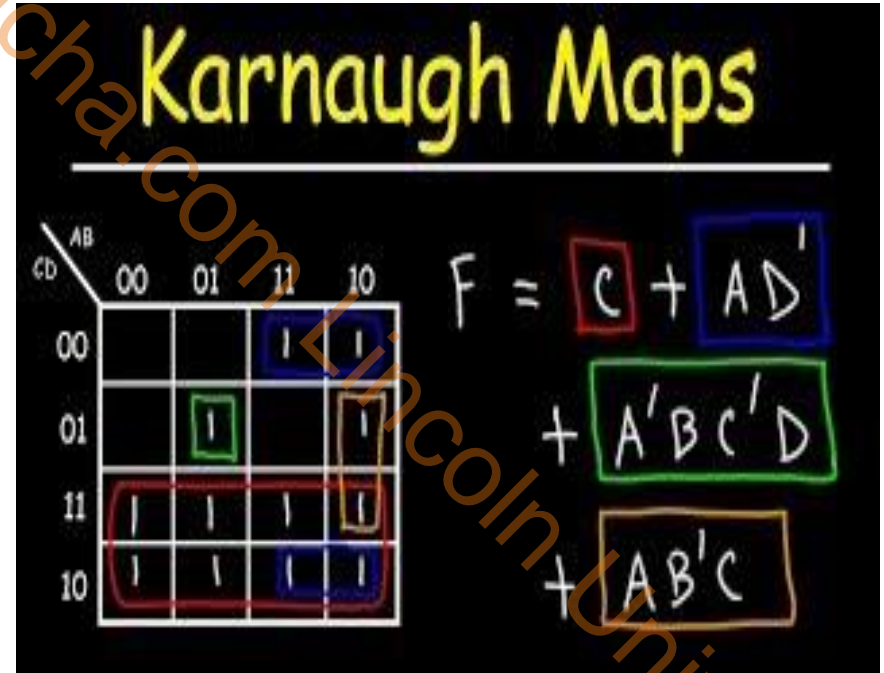Mastery of variable maps is crucial for engineers and designers working in electronics and computer science.



esikheda.com Lincoln University

UNIT 4: COMBINATIONAL LOGIC

Introduction To Combinational Circuit Design Procedure


esikhcha.com Lincoln University

Introduction to Combinational Circuits

Combinational circuits are fundamental building blocks in digital electronics.

They produce outputs based solely on the current inputs without any memory elements.

 Examples include adders, multiplexers, and decoders.




Characteristics of Combinational Circuits

Combinational circuits do not have any feedback loops or storage elements.

The output is a function of the present input values only.

 These circuits can be analyzed and designed using Boolean algebra.




Basic Components of Combinational Circuits

Fundamental components include logic gates like AND, OR, and NOT gates.

These gates can be combined in various ways to create complex functions.

 Each gate performs a specific logical operation to process input signals.




Design Procedure Overview

The design procedure for combinational circuits involves several key steps.

These steps ensure that the circuit meets the desired functionality and specifications.

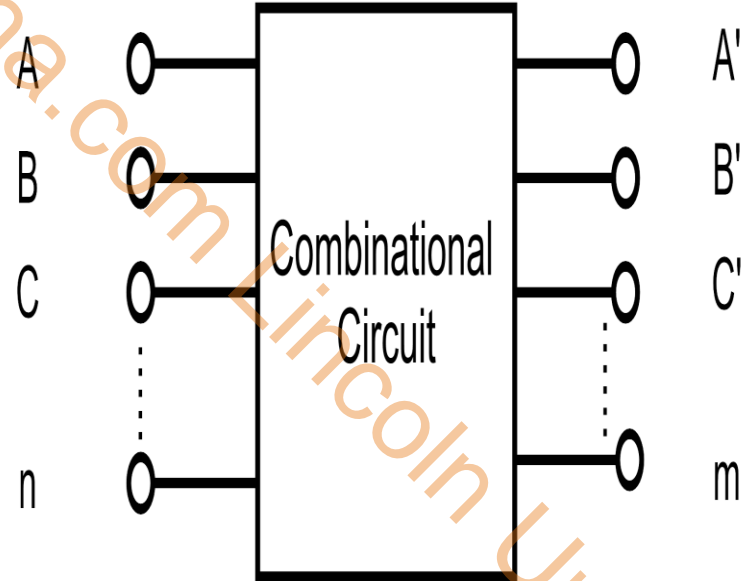A structured approach helps in minimizing errors during the design process.




Step 1 - Define the Problem Statement

Clearly outline the functionality that the circuit needs to achieve.

Identify the number of inputs and outputs based on the requirements.

 Gather all necessary specifications to guide the design process.




**DEFINE THE
PROBLEM**

Step 2 - Create Truth Table

A truth table lists all possible input combinations and their corresponding outputs.

This table serves as a foundation for deriving the logic expressions.

 It provides a clear representation of how the circuit should behave.




Step 3 - Derive Boolean Expressions

Use the truth table to formulate Boolean expressions for the outputs.

Apply Boolean algebra simplification techniques to optimize the expressions.

This step helps in reducing the number of gates required in the circuit.

 b) Write Boolean expressions and construct the truth table describing the outputs of the circuit depicted by the following logic diagram: [2+2=4 marks]




Step 4 - Implement Using Logic Gates

Based on the simplified Boolean expressions, select appropriate logic gates.

Arrange the gates to construct the circuit diagram as per the logic functions.

 Ensure that the connections reflect the derived expressions accurately.




Step 5 - Test and Validate the Circuit

Simulate the circuit using software tools to verify its functionality.

Check if the output matches the expected results for all input combinations.

 Make necessary adjustments if any discrepancies are found during testing.




Conclusion and Applications

Combinational circuits are essential in various digital systems and applications.

Their design procedure ensures reliability and efficiency in circuit performance.

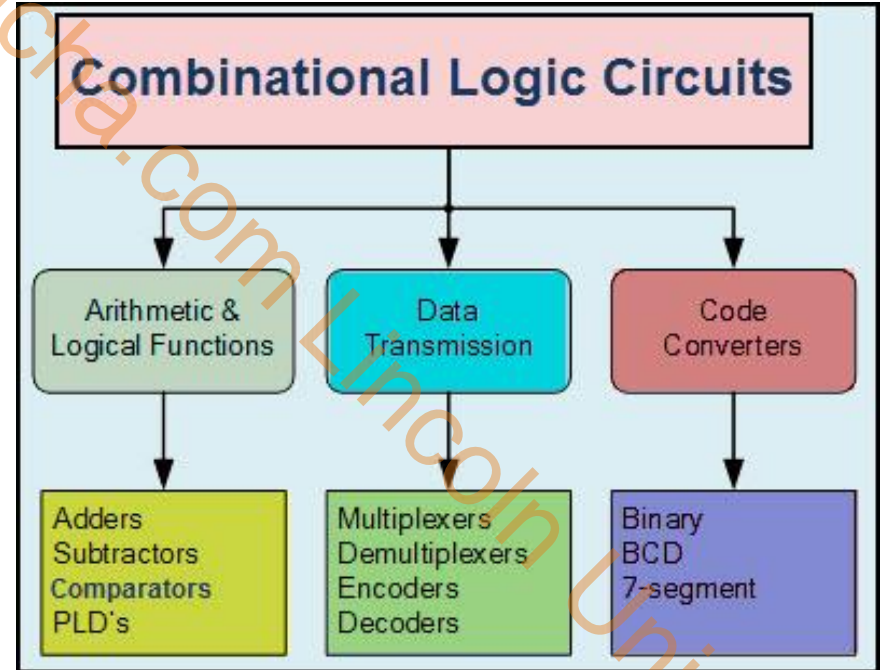Mastering combinational circuit design is crucial for success in electronics engineering.



Code Conversion ☐ Analysis Procedure


esikhcha.com Lincoln University

Introduction to Code Conversion

Code conversion refers to the process of transforming code from one programming language or format to another.

This procedure is essential in modern software development to facilitate interoperability and reuse of existing code.

 Understanding the analysis procedure is crucial for ensuring accuracy and efficiency in code conversion tasks.




Importance of Code Conversion

Code conversion enables organizations to modernize their applications without starting from scratch.

It helps in integrating legacy systems with newer technologies, improving overall system performance.

 Effective code conversion can lead to cost savings and faster time-to-market for new features.




esikhcha.com Lincoln University

Overview of the Analysis Procedure

The analysis procedure for code conversion involves several key steps to ensure a smooth transition.

It begins with identifying the source and target languages or formats for conversion.

 A thorough understanding of both languages is critical for successful code mapping and transformation.




Requirement Gathering

Requirement gathering is the first step in the analysis procedure where developers collect necessary information.

This includes understanding the functionality of the existing code and the desired outcomes in the target language.

 Engaging stakeholders during this phase is essential for capturing all necessary requirements.



Code Assessment

Code assessment involves reviewing the existing codebase for complexity and potential conversion challenges.

This step may include identifying dependencies, third-party libraries, and specific language features used.

A comprehensive code assessment helps in planning the conversion strategy effectively.



Mapping Source to Target

Mapping source code to target code is a crucial part of the analysis procedure.

Developers need to identify equivalent constructs, functions, and libraries in the target language.

This mapping process ensures that the functionality of the original code is preserved in the new environment.


	A	B	C	D	E	F	G	H	I	J	K
1	Client ID	Group ID	Branch ID	Centre ID	Credit Officer ID	Date Joined (DD.MM.YYYY)	First Name	Last Name	Date of Birth (DD.MM.YYYY)	Gender (M/F)	Address 1
2	CL000001	GR000001	1	CE000001	4	11.12.2006	Lucile	Felix Salgo	11.01.1955	F	Calle Guadalupe 34
3	CL000002	GR000002	11			11.12.2006	Irene	Moses Burundi	07.09.1958	F	Royal Avenue 3
4	CL000003	GR000003	12			12.12.2006	John	Mary Watson	28.12.1982	M	Sunrise Blvd 76
5	CL000004	GR000004	21			12.12.2006	Fred	Joseph Conrad	09.07.1970	F	Aggra Hotel 45
6	CL000005	GR000005	31			09.03.2007	Sophie	Eustace Ear	14.03.1983	F	Kinderplatz 158
7	CL000006	GR000006	1	CE000001	4	09.03.2007	Mary	Joseph Connor	03.05.1967	F	Simon Square 85
8	CL000007	GR000007	11		11	26.03.2007	Manuela	Jensha Tish	06.02.1973	F	Plaza Rueda 5
9	CL000008	GR000008	12			28.03.2007	Petra	Ann Sugar	10.09.1966	F	Africa street 91
10	CL000009	GR000009	21			28.03.2007	Sylvie	Geoffrey Assert	08.08.1953	F	Calle Guadalupe 56
11	CL000010	GR000010	31			28.03.2007	Natale	Judith Jonas	13.02.1971	F	Sunrise Blvd 76
12	CL000011	GR000011	1	CE000001	3	29.03.2007	Macarena	Julius Pluto	21.12.1976	F	Aggra Hotel 45
13	CL000012	GR000012	11			29.03.2007	Eugenia	Jabel Price	04.12.1964	F	Calle Guadalupe 15
14	CL000013	GR000013	12			09.04.2007	Louise	Jackeline House	06.08.1970	F	Plaza Rueda 5
15	CL000014	GR000014	21			12.04.2007	Sunny	Joseph River	21.03.1979	F	Kinderplatz 158
16	CL000015	GR000015	31			23.04.2007	Lorene	Stanley Ocean	15.12.1974	F	Calle Duero 324
17	CL000016	GR000016	1	CE000001	4	23.04.2007	Anne	Ephraim Wood	03.10.1972	F	Simon Square 85
18	CL000017	GR000017	11			23.04.2007	Pamela	Ibrahim Modis	01.10.1979	F	Royal Avenue 3
19	CL000018	GR000018	12			27.04.2007	Carmen	Samson Besser	28.03.1970	F	Africa street 91
20	CL000019	GR000019	21			27.04.2007	Lucas	Kipchir Jung	24.09.1976	M	Calle Ebro 45
21	CL000020	GR000020	31			27.04.2007	Pauline	Baltasar Nig	28.04.1968	F	Simon Square 85
22	CL000021	GR000021	1	CE000001	4	14.05.2007	Philp	Patrick Fort	05.07.1978	M	Sunrise Blvd 76
23	CL000022	GR000022	11		11	16.05.2007	Peter	Kam Ulla	07.04.1966	M	Royal Avenue 3
24	CL000023	GR000023	12			16.05.2007	Jennifer	Abdi Vitali	25.09.1965	F	Simon Square 85
25	CL000024	GR000024	21			17.05.2007	Pasi	Albert Wings	03.03.1969	M	Aggra Hotel 45
26	CL000025	GR000025	31			23.05.2007	Roderick	Devash Lopagan	02.08.1968	M	Africa street 91
27	CL000026	GR000026	1	CE000001	3	23.05.2007	Bruce	David Tagalo	15.02.1967	M	Calle Guadalupe 34
28	CL000027	GR000027	11			31.05.2007	Clark	Nyeki Gaspar	11.10.1977	M	Plaza Rueda 5
29	CL000028	GR000028	12			04.06.2007	Veronica	James Fiori	29.12.1953	F	Royal Avenue 3
30	CL000029	GR000029	21			04.06.2007	Christine	Salma River	06.02.1968	F	Simon Square 85
31	CL000030	GR000030	31			06.06.2007	Jason	Kamule Timba	17.04.1981	M	Africa street 91
32	CL000031	GR000031	1	CE000001	4	06.06.2007	Veza	Winifred Arbe	26.04.1970	F	Sunrise Blvd 76

Addressing Language Differences

Different programming languages often have unique paradigms and structures that must be accounted for.

It is essential to analyze language-specific features such as memory management, error handling, and concurrency.

 Addressing these differences early on can prevent issues during the actual conversion process.




Testing and Validation Planning

Planning for testing and validation is integral to the code conversion analysis procedure.

This involves outlining test cases that will verify the correctness of the converted code against the original.

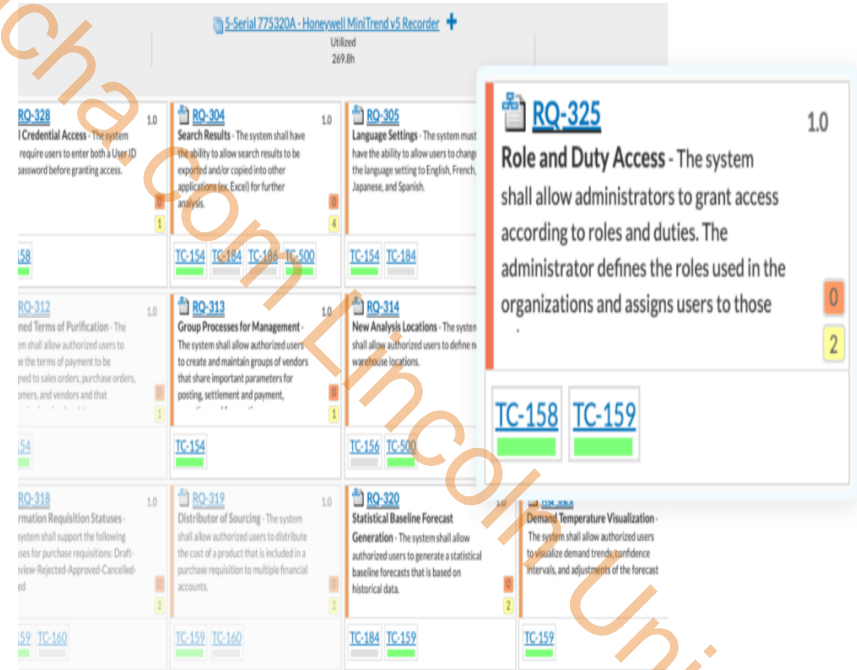Establishing a clear validation strategy helps in identifying discrepancies and ensuring quality assurance.



Documentation and Knowledge Transfer

Proper documentation of the analysis procedure is vital for future reference and team collaboration.

It includes documenting decisions made, challenges encountered, and solutions implemented during the conversion.

Knowledge transfer sessions can help share insights and best practices among team members.



Proper Documentation Vital for Bite Wounds to Prevent Infection

According to the Centers for Disease Control and Prevention (CDC), around 1% of all emergency healthcare visits are due to animal bites. It is also estimated that between 5% and 60% of all bite wounds can be complicated by infection. In order to prevent such infections, adequate initial evaluation and appropriate management of bite wounds is required. Accurate and comprehensive documentation helps wound care physicians understand bite wounds better and perform early wound cleansing and evaluation of injured structures to ensure proper wound management. With wound-specific templates, **wound EMR** facilitates efficient documentation.

Bite Wound Documentation

There are several risk factors that lead to a higher rate of infection of bite wounds -- age (below 2 and above 50), chronic alcohol consumption, use of immunosuppressive drugs and so on. Wound care nurses should gather the history, wound details and other complications of the patient once they are admitted to keep a tab on these risk factors and provide appropriate treatment as soon as possible. Bite wound documentation should include:




Conclusion and Best Practices

In conclusion, a structured analysis procedure is essential for successful code conversion projects.

Adopting best practices, such as thorough documentation and stakeholder involvement, can enhance outcomes.

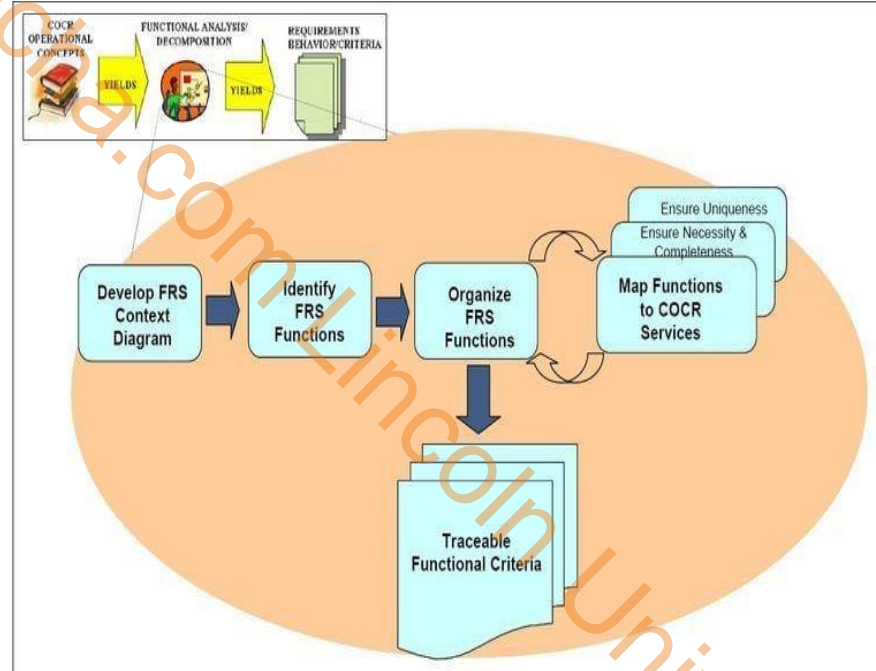Continuous learning and adaptation will ensure improved processes for future code conversion efforts.



Obtaining Truth-Table From Logic Diagram ☐
NAND, NOR And Ex-OR Circuits


esikhcha.com
Lincoln University

Introduction to Logic Diagrams


Logic diagrams are graphical representations of logical expressions.

They use various symbols to represent different logic gates including NAND, NOR, and Ex-OR.

 
Understanding how to derive truth tables from these diagrams is essential in digital electronics.



 
A and B high or C high will make the output high.




 
A or B high and C high will make the output high.



 A low or B high will make the output high.



  The long bar above the output means that the output goes low when A or B go high.



Understanding NAND Gates

The NAND gate is a universal gate that outputs false only when all inputs are true.

Its symbol consists of an AND gate followed by a NOT operation.

The truth table for a NAND gate can be derived by noting the output conditions for its inputs.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table for NAND Gates

The truth table for a NAND gate has two inputs (A and B) and one output (Y).

The possible input combinations are (0,0), (0,1), (1,0), and (1,1).

The corresponding outputs for these combinations are 1, 1, 1, and 0, respectively.




A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Understanding NOR Gates

The NOR gate is another universal gate that outputs true only when all inputs are false.

Its symbol combines that of an OR gate followed by a NOT operation.

 Like NAND, the truth table for a NOR gate can be easily derived from its input combinations.



Truth Table for NOR Gates

The truth table for a NOR gate also has two inputs (A and B) and one output (Y).

The combinations of inputs remain the same: (0,0), (0,1), (1,0), and (1,1).

The outputs for these combinations are 1, 0, 0, and 0, respectively.




A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Understanding Ex-OR Gates

The Ex-OR (Exclusive OR) gate outputs true when the number of true inputs is odd.

Its symbol is distinct, often resembling an OR gate with an additional curved line.

 The truth table for an Ex-OR gate can also be derived from analyzing its unique output behavior.




Truth Table for Ex-OR Gates

The truth table for an Ex-OR gate has two inputs (A and B) and one output (Y).

The input combinations remain the same as previous gates: (0,0), (0,1), (1,0), and (1,1).

The outputs for these combinations are 0, 1, 1, and 0, respectively.

NOR GATE

 

TRUTH TABLE


INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

Deriving Truth Tables from Logic Diagrams

To derive a truth table from a logic diagram, start by identifying the gates and their connections.

List all possible combinations of inputs for the circuit being analyzed.

 Calculate the output for each combination step-by-step according to the gates' functions.




esikhcha.com Lincoln University

Example Circuit Analysis

Consider a circuit with a NAND gate followed by an Ex-OR gate.

Begin with the input combinations and evaluate the output of the NAND gate first.

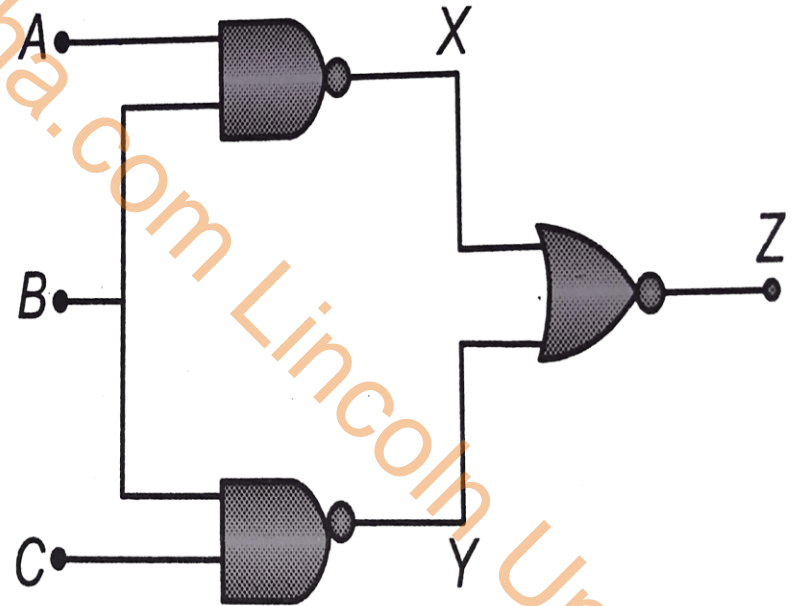Use the output from the NAND gate as an input to the Ex-OR gate to complete the truth table.



Conclusion and Applications

Understanding truth tables is crucial for designing and analyzing digital circuits.

Logic gates like NAND, NOR, and Ex-OR are fundamental building blocks in electronics.

Mastery of truth tables enhances problem-solving skills in digital logic design and analysis.

A logic circuit has 4 inputs, each of which can have a value of either 0 or 1.
How many rows would you have to add to a truth table in order to show all of the different possible combinations of these inputs?

Truth table:

1st Input	2nd Input	3rd Input	4th Input	Output
0	0	0	0	
0	0	0	1	
0	0	1	0	
⋮	⋮	⋮	⋮	

2 inputs:
 $2 \times 2 = 2^2$

4 inputs: combinations = $2 \times 2 \times 2 \times 2$
 $= 2^4 = 16$

- 4 inputs
- each has 2 possible values
- inputs are independent

n inputs with 2 possible values each:
 2^n combinations

UNIT 5: COMBINATIONAL LOGIC WITH MSI & LSI

esikhona.com
Lincoln University

**Introduction To MSI And LSI Binary Adder
Decimal Adder**


esikhcha.com Lincoln University

Introduction to MSI and LSI

MSI stands for Medium Scale Integration, which integrates hundreds of transistors on a single chip.

LSI stands for Large Scale Integration, which integrates thousands of transistors on a single chip.

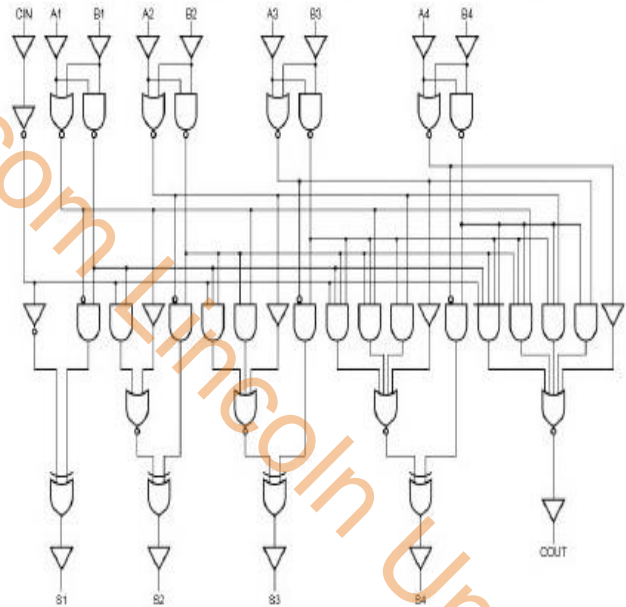Both technologies have revolutionized the design and efficiency of digital circuits and systems.




Importance of MSI and LSI

They allow for complex circuits to be miniaturized, saving space and reducing costs.

These technologies enable the production of reliable components with high performance.

 MSI and LSI are fundamental in the development of modern computing devices and systems.



Overview of Binary Adders

A binary adder is a digital circuit that performs the addition of binary numbers.

The most basic type is the half adder, which adds two single-bit binary numbers.

Full adders can be combined to create adders for larger binary numbers.

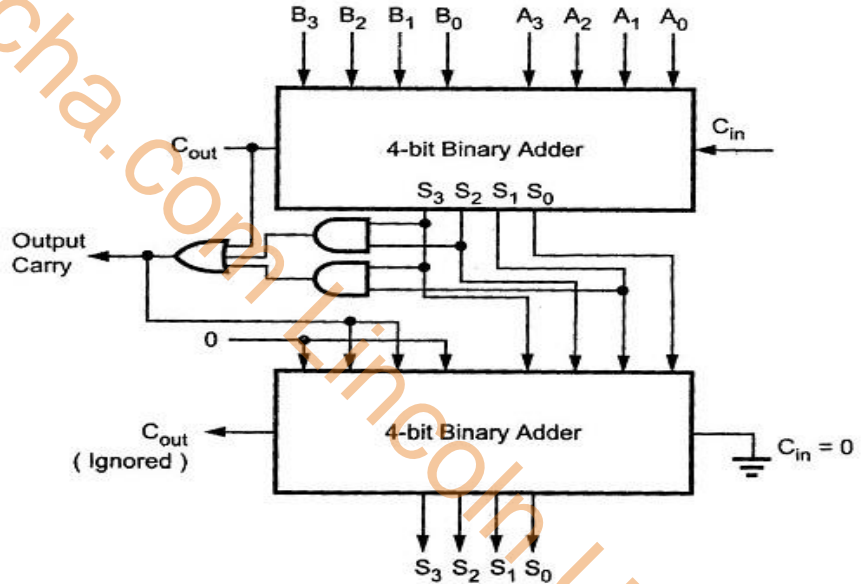



Fig. 3.32 Block diagram of BCD adder

Half Adder Design

A half adder has two inputs and produces two outputs: the sum and the carry.

The sum output represents the result of the addition without carry, while the carry output indicates overflow.

 The logic gates used in a half adder are an XOR gate for the sum and an AND gate for the carry.




Full Adder Design

A full adder combines two input bits and a carry-in bit to produce a sum and a carry-out.

It consists of two half adders and an OR gate to manage the carry outputs.

 Full adders enable the addition of multi-bit binary numbers by chaining them together.



Applications of Binary Adders

Binary adders are used in arithmetic logic units (ALUs) within CPUs for calculations.

They play a crucial role in digital signal processing for operations like filtering and modulation.

Binary adders are fundamental components in calculators and various digital devices.

Arithmetic and Logic Units (or ALUs) are found at the core of microprocessors, where they implement the arithmetic and logic functions offered by the processor (e.g., addition, subtraction, ANDing two values, etc.). An ALU is a combinational circuit that combines many common logic circuits in one block. Typically, ALU inputs are comprised of two N -bit buses, a carry-in, and M select lines that select between the 2^M ALU operations. ALU outputs include an N -bit bus, a function output and a carry out.

 


Figure 1. Arithmetic and logic units.

Since ALUs operate on binary numbers, the bit-slice design method is indicated. ALU design should follow the same process as other bit-slice designs: first, define and understand all inputs and outputs of a bit slice (i.e., prepare a detailed block diagram of the bit slice); second, capture the required logical relationships in some formal method (e.g., a truth table); third, find minimal circuits (by using K-maps or Espresso) or write VHDL code; and fourth, proceed with circuit design and verification.



Figure 2. ALU bit-sliced block.

OpCode	Description	Carry	F
000	Addition	$A + B + C_{in} = (A \oplus B)$	$A \oplus B \oplus C_{in}$
001	Increment	$A + C_{in}$	$A \oplus C_{in}$
010	Subtract	$A - B + C_{in} = (A \oplus B)$	$A \oplus B \oplus C_{in}$
011	No Operation	0	0
100	Bit-wise XOR	0	$A \oplus B$
101	Bit-wise Inversion	0	\bar{A}
110	Bit-wise OR	0	$A + B$
111	Bit-wise AND	0	$A \cdot B$

 


Figure 3. Block diagram of ALU composed of bit-sliced blocks

A block diagram and operation table for our ALU is shown above. Note in the operation table, entered variables are used to define the functional requirements for the two outputs (F and Cout) of the bit-slice module.

Once the ALU operation table is complete, a circuit can be designed following any one of several methods: K-maps can be constructed and minimal circuits can be looped; muxes can be used (with an 8:1 mux for F and a 4:1 mux for Cout); the information could be entered into a computer-based minimizer and the resulting equations implemented directly; or we could bypass all the difficult and error-prone structural work and create a behavioral description using a hardware description Language (such as Verilog or VHDL).

Using the bit-slice method, design the VHDL circuit of the ALU described in the operation table and block diagram above.

Overview of Decimal Adders

A decimal adder is designed to add decimal numbers and is often used in digital devices.

It differs from binary adders by dealing with base-10 numbers, which include digits 0-9.

Decimal adders ensure that the results stay within the realm of decimal digits by managing carry operations.

1. For adding 4 bit numbers we need _____ full adders connected in parallel. The largest decimal number which this adder can add is _____.

2. A full adder consists of _____ (Choose the correct option)

- a) Two half adders cascaded together
- b) Two half adders and one OR gate
- c) Two half adders and one AND gate
- d) Two NAND gates

3. What is another name for carry out? _____

- a) Register control bit
- b) overflow bit
- c) MSB
- d) underflow bit

4. Which Boolean expression describes the sum bit of a full adder? _____

- a) $A_i \text{ XOR } B_i \text{ XOR } C_i$
- b) $A_i B_i + A_i C_i + B_i C_i$

5. Which binary addition below has an error?

Ans: _____

a)
$$\begin{array}{r} 0\ 1\ 1 \\ 1\ 0\ 1\ 1 \\ +\ 1\ 0\ 1\ 1 \\ \hline 1\ 0\ 1\ 1\ 0 \end{array}$$
 <-- carries
<-- first number
<-- second number
<-- result

b)
$$\begin{array}{r} 1\ 1\ 1 \\ 1\ 0\ 0\ 1 \\ +\ 1\ 1\ 1\ 1 \\ \hline 1\ 1\ 0\ 0\ 0 \end{array}$$
 <-- carries
<-- first number
<-- second number
<-- result

c)
$$\begin{array}{r} 0\ 1\ 0 \\ 1\ 0\ 1\ 0 \\ +\ 0\ 1\ 1\ 0 \\ \hline 1\ 1\ 0\ 0 \end{array}$$
 <-- carries
<-- first number
<-- second number
<-- result


Design of Decimal Adders

Decimal adders can be built using multiple binary adders while incorporating correction for decimal values.

They often use a series of binary adders followed by a correction mechanism to adjust for carry values.

The design complexity increases with the need to manage the range of decimal values.

Full Adder - Circuit

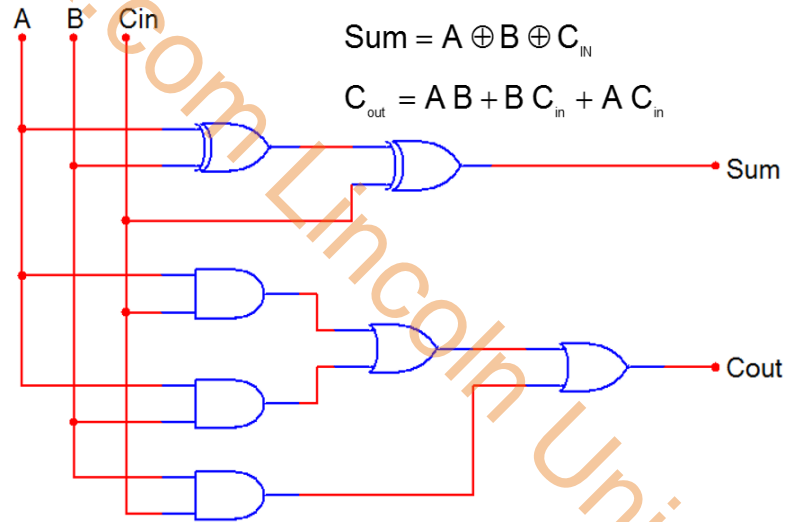

Applications of Decimal Adders

Decimal adders are commonly used in calculators to perform arithmetic operations accurately.


They are essential in financial and business applications where decimal arithmetic is crucial.

Decimal adders are also used in various electronic devices that require human-readable outputs.

```
# Python Program to Perform Arithmetic Operations
num1 = float(input(" Please Enter the First Value Number 1: "))
num2 = float(input(" Please Enter the Second Value Number 2: "))
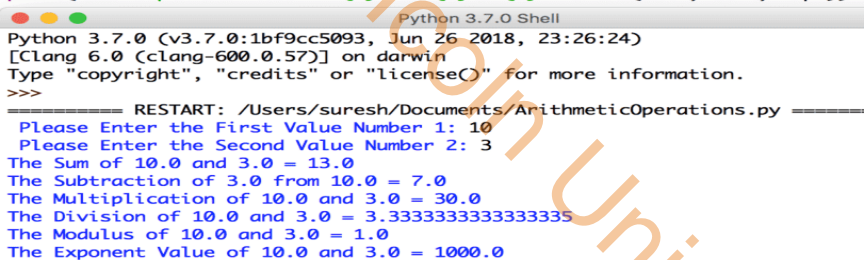
# Add Two Numbers
add = num1 + num2
# Subtracting num2 from num1
sub = num1 - num2
# Multiply num1 with num2
multi = num1 * num2
# Divide num1 by num2
div = num1 / num2
# Modulus of num1 and num2
mod = num1 % num2
# Exponent of num1 and num2
expo = num1 ** num2

print("The Sum of {0} and {1} = {2}".format(num1, num2, add))
print("The Subtraction of {0} from {1} = {2}".format(num2, num1, sub))
print("The Multiplication of {0} and {1} = {2}".format(num1, num2, multi))
print("The Division of {0} and {1} = {2}".format(num1, num2, div))
print("The Modulus of {0} and {1} = {2}".format(num1, num2, mod))
print("The Exponent Value of {0} and {1} = {2}".format(num1, num2, expo))
```



```
Python 3.7.0 Shell
Python 3.7.0 (v3.7.0:1bf9cc5093, Jun 26 2018, 23:26:24)
[Clang 6.0 (clang-600.0.57)] on darwin
Type "copyright", "credits" or "license()" for more information.
>>>
===== RESTART: /Users/suresh/Documents/ArithmeticOperations.py =====
 Please Enter the First Value Number 1: 10
 Please Enter the Second Value Number 2: 3
The Sum of 10.0 and 3.0 = 13.0
The Subtraction of 3.0 from 10.0 = 7.0
The Multiplication of 10.0 and 3.0 = 30.0
The Division of 10.0 and 3.0 = 3.3333333333333335
The Modulus of 10.0 and 3.0 = 1.0
The Exponent Value of 10.0 and 3.0 = 1000.0
```

Conclusion and Future Trends

MSI and LSI technologies have significantly advanced digital circuit design and efficiency.

The development of adders continues to evolve with the need for faster and more efficient computational methods.

Future trends may include the integration of quantum computing principles to enhance addition operations.



**BCD Adder ☐ Magnitude Comparator ☐ Decoders
And Encoders**


esikhcha.com Lincoln University

Introduction to BCD Adder, Magnitude Comparator, Decoders and Encoders

This presentation will cover key digital components in computer systems.

We will explore the functionality and applications of BCD adders, magnitude comparators, decoders, and encoders.

 Understanding these components is essential for designing efficient digital circuits.



What is a BCD Adder?

A BCD adder is a digital circuit that performs addition on Binary-Coded Decimal numbers.

It corrects any invalid BCD results by adding a fixed value when the sum exceeds 9.

This ensures that the output remains a valid BCD representation after each addition operation.

8. An adder circuit performs arithmetic addition using binary numbers. You are to design a 2-bit adder (adds two 2-bit numbers). Complete the truth table below to characterize the behavior of the circuit. Generate maximally simplified SOP and POS expressions for each of the three outputs (Carry, Sum1 and Sum0).

Example: if B = 01 and A = 11 then B plus A = 100

B1	B0	A1	A0	Carry	Sum1	Sum0
0	0	0	0	0	0	0
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1	1	0	0
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

Functionality of BCD Adder

The BCD adder consists of a standard binary adder and additional logic gates.

It generates a carry output when the result exceeds the maximum value of 9 in BCD.

The correction logic adds 6 (0110) to the binary sum whenever a carry is generated.

1. Using only logic gates, design a 2-bit full adder with carry. Here is a partial truth table for the circuit.

INPUTS					OUTPUTS		
A0	A1	B0	B1	Ci	S0	S1	Co
0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0
0	1	0	0	0	0	1	0
1	0	1	0	0	0	1	0
0	1	0	1	0	0	0	1
0	1	0	0	1	1	1	0
1	0	1	0	1	1	1	0
1	1	1	1	1	1	1	1

Where A and B are inputs, Ci is carry in, Si is output and Co is carry out.

Draw a schematic showing the gate interconnections. Include either a boolean equation or an explanation of your design that matches the schematic you submit.

What is a Magnitude Comparator?

A magnitude comparator is a digital circuit that compares two binary numbers.

It determines whether one number is greater than, less than, or equal to another.

The output typically consists of three signals indicating the comparison result.

A magnitude comparator compares two binary numbers and determines if one number is greater than, less than, or equal to the other number. If two binary numbers are considered as A and B, the magnitude comparator gives three outputs for $A > B$, $A < B$, and $A = B$. Design a circuit to realize this function for two 4-bit binary numbers through the following steps.


- Construct truth table
 - Derive and simplify Boolean functions
 - Draw the gate expression
- please show clear steps

Functionality of Magnitude Comparator

Magnitude comparators use logic gates to evaluate the bits of the two numbers.

They output signals for less than ($A < B$), equal to ($A = B$), and greater than ($A > B$).

 Comparators can handle binary inputs of different lengths by zero-padding the shorter input.




Logic Circuit of 2-bit Magnitude Comparator

Applications of Magnitude Comparator

Magnitude comparators are essential in digital circuits for decision-making processes.

They are used in sorting algorithms and data routing systems to optimize performance.

 Comparators are also relevant in arithmetic logic units (ALUs) for comparison operations.



What are Decoders?

A decoder is a combinational circuit that converts binary input signals into a unique output signal.

It typically has 2^n inputs and n outputs, where n is the number of bits in the input.

The active output corresponds to the binary value represented by the input signals.


TASK #3

Task #3 - Building a 3 x 8 Decoder

A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n output lines. For instance, a 2×4 decoder has 2 inputs and 4 outputs. Decoders also have an enable input. Build a 3×8 decoder with an enable that is asserted (or active) high and outputs that are asserted (or active) high. Data inputs are to be C, B, A where C is the MSB. Enable is to be EN. The outputs are to be Y7, Y6, Y5, Y4, Y3, Y2, Y1, and Y0.

Build this circuit. Test this circuit. You may use the Combinational Analysis tools in Logisim to help you on this circuit. Name it as 3x8DECODER. In your lab report include:

 - Truth table
- K map (if necessary) and reduced equations
- C,B,A,EN = 1001 as a test case
- C,B,A,EN = 1000 of the truth table as a test case



Prepare the device symbol called 3x8DECODER. In your lab report include:


- C,B,A,EN = 0101 of the truth table as a test case
- An explanation of how decoders work or function
- Include all detailed design to support your circuit (schematics, truth tables, k-maps, equations, etc).

Functionality and Types of Decoders

Decoders can be classified into binary decoders, BCD decoders, and 3-to-8 line decoders.

They use AND, OR, and NOT gates to produce outputs based on input combinations.

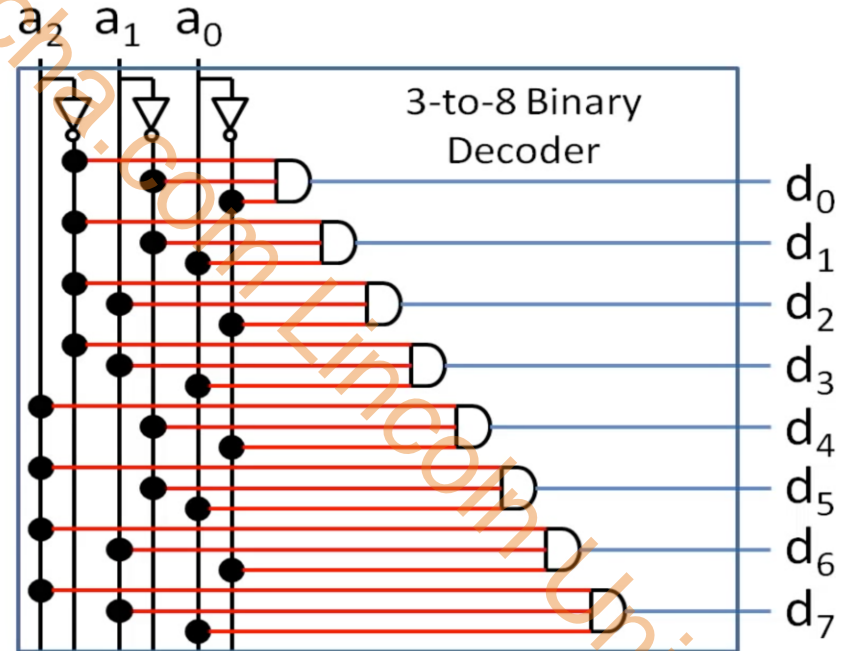A common application is in memory address decoding, where a specific address activates corresponding memory chips.



What are Encoders?

An encoder is a combinational circuit that converts multiple input signals into a smaller number of output signals.

It effectively performs the reverse function of a decoder, representing inputs in binary format.

Encoders are often used in applications like keyboards and data compression systems for efficient data handling.

A combinational circuit converts a BCD input (ABCD) into an Excess-3 output (WXYZ). All invalid combinations are don't cares. Implement the X output using the OR-NAND two level form and the Y input using NAND-AND DO NOT IMPLEMENT W OR Z!

Multiplexers ? **Types Of ROM** ? **Programmable
Logic Array (PLA)**

Introduction to Multiplexers

A multiplexer, or MUX, is a device that selects one of many input signals and forwards the selected input to a single output line.

By using control signals, multiplexers can effectively manage multiple data lines, enhancing circuit efficiency.

Multiplexers are widely used in communication systems, data routing, and complex digital circuits.

What is Multiplexer....?


- A **multiplexer** (or **mux**) is a device that selects one of several analog or digital input signals and forwards the selected input into a single line.
- A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output.
- It is also called a **data selector**.

Functionality of Multiplexers

The basic function of a multiplexer is to reduce the number of data lines needed for transmission.

It operates by using control lines that determine which input to connect to the output.

 A common example is the 2-to-1 multiplexer, which has two inputs, one output, and one control line.



Types of Multiplexers

Multiplexers can vary in size, including 2-to-1, 4-to-1, 8-to-1, and more complex configurations.

They can also be categorized based on their applications, such as analog multiplexers and digital multiplexers.

Each type serves specific purposes in simplifying circuit design and enhancing functionality.

Analog Switch Multiplexers Market Provides a Comprehensive Analysis Including a Macro Overview of the Market as well as Micro Details such as Market Size and Competitive Landscape

Analog Switch Multiplexers Market Analysis and Latest Trends

Analog Switch Multiplexers are devices used to switch multiple analog signals to a single or multiple output channels. These devices are commonly used in applications such as data acquisition systems, communication systems, test and measurement equipment, and audio/video equipment. The Analog Switch Multiplexers Market is expected to grow at a CAGR of 3.80% during the forecast period.

The growth of the Analog Switch Multiplexers Market can be attributed to the increasing demand for efficient signal switching devices in various industries. The rising adoption of Analog Switch Multiplexers in automotive electronics, consumer electronics, and telecommunications is also driving market growth. Additionally, advancements in technology and the development of new applications are expected to fuel the growth of the Analog Switch Multiplexers Market in the coming years.

Some of the latest trends in the Analog Switch Multiplexers Market include the integration of advanced features such as low on-resistance, low power consumption, and high bandwidth. Manufacturers are focusing on developing compact and cost-effective Analog Switch Multiplexers to cater to the growing demand from end-users. Furthermore, the increasing use of Analog Switch Multiplexers in IoT devices and automation systems is expected to create lucrative opportunities for market players in the near future.

Get a Sample PDF of the Report: <https://www.reportprime.com/enquiry/request-sample/1424>

Analog Switch Multiplexers Major Market Players

The analog switch multiplexers market is highly competitive with key players such as Maxim Integrated, Diodes Inc, Texas Instruments, Renesas Electronics, Amphenol, ON Semiconductor, Nxpperia, STMicroelectronics, Broadcom, Conesys, Renesas Electronics Corporation, Microchip, Molex, MPS, NXP, Pulse Electronics, Quectel Wireless Solutions, Rochester Electronics, ROHM, Toshiba, and Vishay competing for market share.

Among these players, Maxim Integrated is a leading provider of analog switch multiplexers. The company has a strong market presence and offers a wide range of analog switch multiplexers for various applications. Maxim Integrated has been focusing on expanding its product portfolio and enhancing its technological capabilities to meet the evolving needs of customers.

Another key player in the market is Texas Instruments, which is known for its high-quality analog switch multiplexers. The company has a strong market position and a global presence, catering to a diverse range of industries. Texas Instruments has been investing in research and development to drive innovation and stay ahead of the competition.

Introduction to ROM

Read-Only Memory (ROM) is a type of non-volatile memory that is used to store firmware or software that is rarely changed.

Unlike RAM, ROM retains its contents even when the power is turned off, making it essential for boot processes.

ROM is crucial in embedded systems, where reliable and permanent data storage is required.



Read Only Memory

Types of ROM

There are several types of ROM, including PROM (Programmable ROM), EPROM (Erasable Programmable ROM), and EEPROM (Electrically Erasable Programmable ROM).

PROM can be programmed only once after manufacturing, while EPROM can be erased and reprogrammed using UV light.

EEPROM allows data to be erased and rewritten electrically, making it versatile for modern applications.




Characteristics of ROM

ROM is characterized by its non-volatility, meaning it does not lose data when power is lost.

It has a slower read speed compared to RAM but is generally more reliable for permanent storage.

 ROM is often used to store system firmware, including the BIOS in computers, ensuring that critical instructions are always available.



Introduction to PLA

A Programmable Logic Array (PLA) is a type of digital device used to implement combinational logic circuits.

PLAs consist of a programmable AND gate array followed by a programmable OR gate array, facilitating flexible logic design.


They are used in applications where specific logic functions need to be tailored or modified.

Programmable logic array example

Multiple functions of A, B, C

- $F1 = A B C$
- $F2 = A + B + C$
- $F3 = A' B' C'$
- $F4 = A' + B' + C'$
- $F5 = A \text{ xor } B \text{ xor } C$
- $F6 = A \text{ xnor } B \text{ xnor } C$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

 


Structure of PLA

The structure of a PLA includes two main parts: the AND plane and the OR plane, allowing for comprehensive logic design.

Programmable connections in both planes enable designers to create custom logic functions based on requirements.

This programmability makes PLAs versatile for various logical operations and optimization.

Internal Structure of a PLA

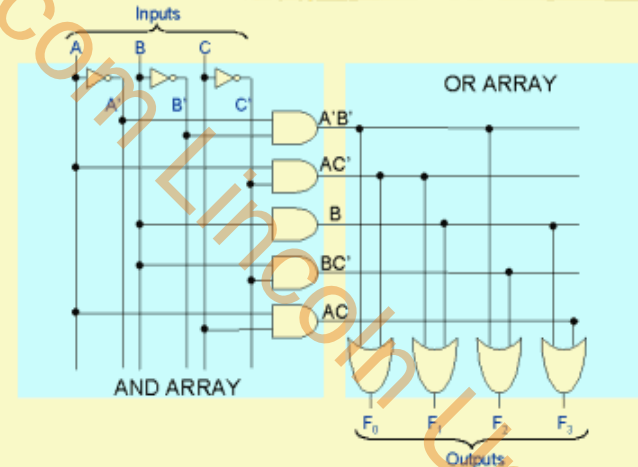


Advantages of PLA

PLAs provide high flexibility, allowing designers to implement complex logic functions without the need for extensive hardware changes.

They can be reprogrammed, making them suitable for prototyping and iterative design processes.

 The compact design of PLAs helps reduce the overall circuit size while maintaining functionality.




Conclusion

Multiplexers, ROM, and PLAs are fundamental components in digital electronics, each serving distinct purposes.

Understanding these components is essential for designing efficient and effective digital systems.

Continuous advancements in these technologies are shaping the future of electronic design and functionality.

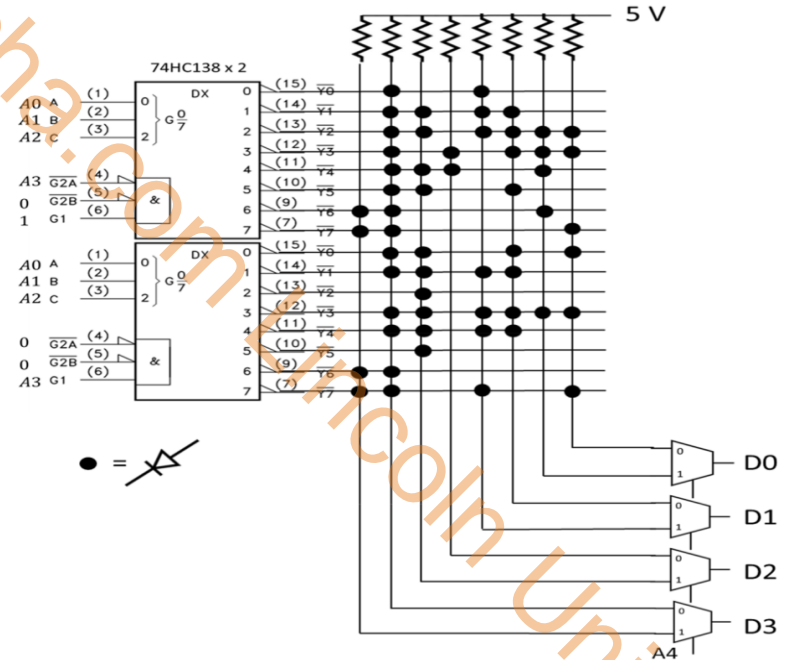

UNIT 6: SEQUENTIAL LOGIC

esikhona.com Lincoln University

Introduction To Sequence ? Flip-Flops ? Point


esikhcha.com Lincoln University

Introduction to Sequences

Sequences are ordered lists of numbers or elements that follow a specific pattern.

They are fundamental in mathematics and computer science for defining relationships and processes.

 Understanding sequences is essential for working with algorithms and programming languages.




Types of Sequences

Sequences can be classified into arithmetic, geometric, and Fibonacci sequences, among others.

Each type of sequence has its unique properties and formulas for determining its terms.

 Identifying the type of sequence is crucial for solving mathematical problems effectively.




- | <i>Vertical</i> | | | <i>Horizontal</i> | | |
|------------------------|------------|-----------------------|-------------------|-----------------------|----------------------|
| 1) 72, 48, 24... | 12TH TERM? | 10) -6, -24, -96... | 16TH TERM? | 1) 212, 106, 0... | 14TH TERM? |
| 2) 72, 48, 32... | 10TH TERM? | 11) 200, 40, 8... | 12TH TERM? | 2) 100, 300, 225... | 27TH TERM? |
| 3) 20, -2, -24... | 23RD TERM? | 12) 2, -10, 50... | 14TH TERM? | 3) -2, 0, -96, 384... | 15TH TERM? |
| 4) 8, -16, 32... | 29TH TERM? | 13) 110, -110, 110... | 32ND TERM? | 4) -10, -17, -24... | 18TH TERM? |
| 5) -1, 5, -25... | 15TH TERM? | 14) 105, -5, -115... | 24TH TERM? | 5) -6, -3, 0... | 15TH TERM? |
| 6) 2, -10, -22... | 32ND TERM? | 15) 10, 120, 230... | 27TH TERM? | 6) -21, 22, 65... | 30TH TERM? |
| 7) 550, 440, 352... | 22ND TERM? | 16) -450, -82, 286... | 21ST TERM? | 7) -1, 5, 11... | 11TH TERM? |
| 8) 16, 92, 846, 423... | 20TH TERM? | 17) -6, -24, -42... | 29TH TERM? | | 14) 1200, 300, 75... |
| 9) 10, 20, 30... | 27TH TERM? | | | | 11TH TERM? |

The Concept of Flip-Flops

Flip-flops are basic building blocks in digital electronics used for storing binary data.

They function as bistable devices, meaning they can exist in one of two stable states.

 Flip-flops are essential for implementing memory elements and sequential circuits.



Types of Flip-Flops

The most common types of flip-flops include SR, JK, D, and T flip-flops.

Each type has distinct characteristics and is used for specific applications in digital circuits.

Understanding the operation of each flip-flop type is vital for designing effective digital systems.

esikhcha.com Lincoln University

Timing Diagrams for Flip-Flops


Timing diagrams visually represent the behavior of flip-flops over time.

They illustrate the relationship between input signals and the resulting output states.


Analyzing these diagrams helps in understanding how flip-flops respond to clock signals.

 5.4 Timing Diagrams for Latch and Flip-Flops

EG-1: Draw the output waveform of a *D latch* given the following *Clk* and *D* inputs:



 EG-2: Draw the output waveform of a *D latch* given the following *Clk* and *D* inputs:



The Role of Clock Signals

Clock signals are crucial for synchronizing the operation of flip-flops in sequential circuits.


They dictate when the state of a flip-flop should change based on input conditions.

Proper clocking ensures reliable operation and timing in digital systems.

Clock

Enable

Output

 


Introduction to Points

In mathematics and computer graphics, a point is a precise location in space.

Points have no dimensions, meaning they have no length, width, or height.

 They are often represented by coordinates in a Cartesian coordinate system.



esikhcha.com Lincoln University

Points in Geometry

Points serve as the foundation for geometric concepts, forming lines, angles, and shapes.

They help define relationships and properties within geometric figures.

Understanding points is essential for higher-level geometry and spatial reasoning.

The image displays a set of four math task cards titled "GEOMETRIC CONCEPTS Math Task Cards" by "The TEACHER next Door". Each card is framed in purple and contains a question related to geometry. The cards are arranged in a 2x2 grid. The top-left card asks to draw a ray and identify the difference between a ray and a line. The top-right card asks to identify lines as parallel, perpendicular, or intersecting, accompanied by a diagram of two intersecting lines. The bottom-left card asks to identify an angle as acute, obtuse, right, or straight, with a diagram of an obtuse angle. The bottom-right card asks to count the number of acute, obtuse, and right angles in a polygon, with a diagram of a trapezoid. A large watermark "esikhcha.com" is visible across the entire image.

GEOMETRIC CONCEPTS
Math Task Cards

GEOMETRIC CONCEPTS
Draw a ray.
What's the difference between a ray and a line?

GEOMETRIC CONCEPTS
Identify the lines as parallel, perpendicular, or intersecting.

GEOMETRIC CONCEPTS
Is the angle acute, obtuse, right, or straight?

GEOMETRIC CONCEPTS
Count the number of acute, obtuse, and right angles inside the polygon.

The TEACHER next Door


Points in Computer Science

In computer science, points can represent data structures and memory addresses.

They are used in algorithms to denote specific locations or values within a dataset.

Efficient manipulation of points is crucial for optimizing performance in programming.

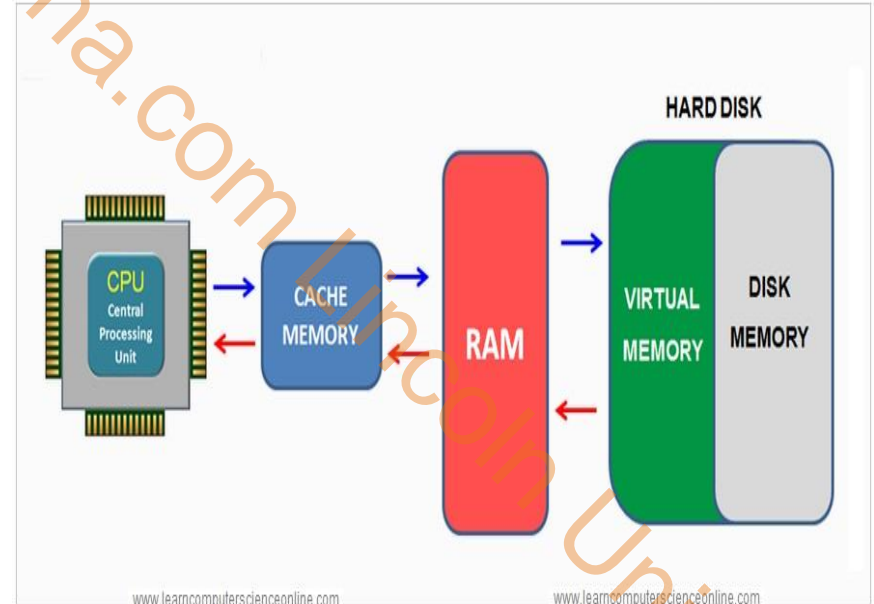Operating System Memory Management - Virtual Memory




Conclusion and Applications

Sequences, flip-flops, and points are interconnected concepts that are fundamental in various fields.

Mastery of these topics enhances problem-solving skills in mathematics and engineering.

 Their applications range from digital circuit design to data analysis in computer programming.



Edge-Triggered Flip-Flop Analysis Of Clocked Sequential Circuits


esikhcha.com Lincoln University

Introduction to Edge-Triggered Flip-Flops

Edge-triggered flip-flops are vital components in digital circuits, primarily used for storing binary data.

They change their output state only on a specific edge of the clock signal, either rising or falling.

 This feature allows for synchronized data sampling and improves the reliability of sequential circuits.



Operation of D Flip-Flop

The D flip-flop captures the value of the D input at the moment of the clock's active edge.

Its output (Q) reflects the D input value until the next clock edge, ensuring stable state retention.

This functionality is crucial in constructing registers and memory cells in digital systems.

Design a dual-edge D flip-flop (i.e., it captures the input signal at both rising and falling clock edges).

Specification

- Data input: D
- Clock input: CK
- Output: Q
- It has a synchronous active-high set input (S).
- It has a synchronous active-low reset input (R).
- S dominates R, i.e., if $S=1$, $Q=1$. If $S=0$ and $R=0$, $Q=0$. If $S=0$ and $R=1$, it is just a dual-edge D-F/F.

Timing Characteristics



Edge-triggered flip-flops have specific timing parameters like setup time, hold time, and clock-to-output delay.

Setup time is the minimum interval before the clock edge that the input must be stable.

Hold time is the duration after the clock edge that the input must remain stable to ensure correct operation.

  3) (10 points) For the following edge-triggered D flip-flops show the timing diagram

- Assume it is a positive-edge-triggered D flip-flop
- Assuming it is a negative-edge-triggered D flip-flop




Analysis of Clocked Sequential Circuits

Clocked sequential circuits are composed of flip-flops and combinational logic that process input signals over time.

The analysis involves understanding state transitions based on input signals and clock cycles.

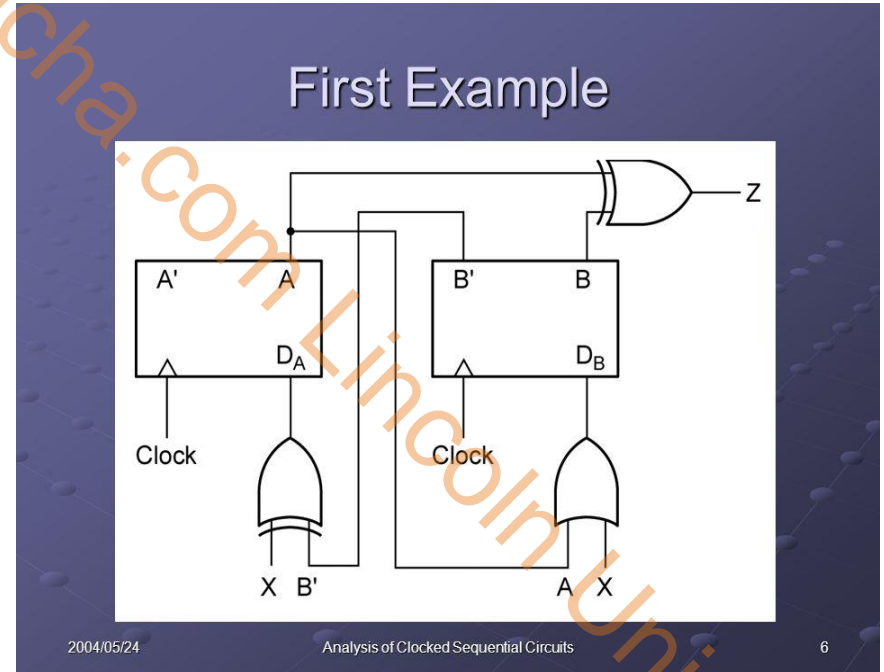These circuits can be designed for various applications, including counters, registers, and state machines.




State Diagrams and State Tables

State diagrams visually represent the possible states of a sequential circuit and the transitions between them.

State tables provide a structured way to summarize the outputs and next states for each current state and input combination.

Both tools aid in designing and debugging sequential circuits by clarifying their operation.

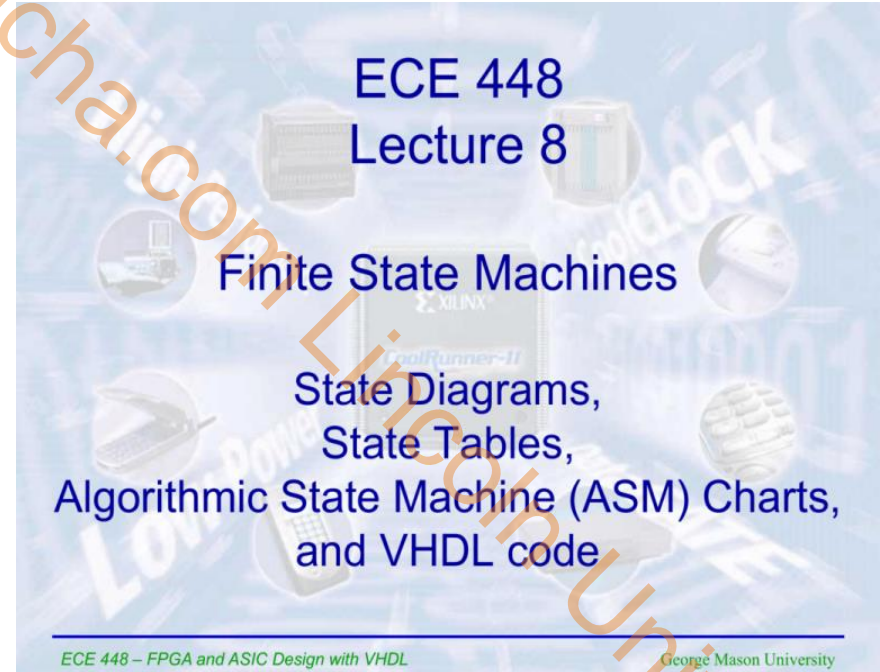

ECE 448
Lecture 8

Finite State Machines

State Diagrams,
State Tables,
Algorithmic State Machine (ASM) Charts,
and VHDL code

ECE 448 – FPGA and ASIC Design with VHDL


George Mason University

Timing Diagrams

Timing diagrams illustrate the relationship between the clock signal and the outputs of the flip-flops.

They are crucial for visualizing how data is captured and propagated through the circuit over time.

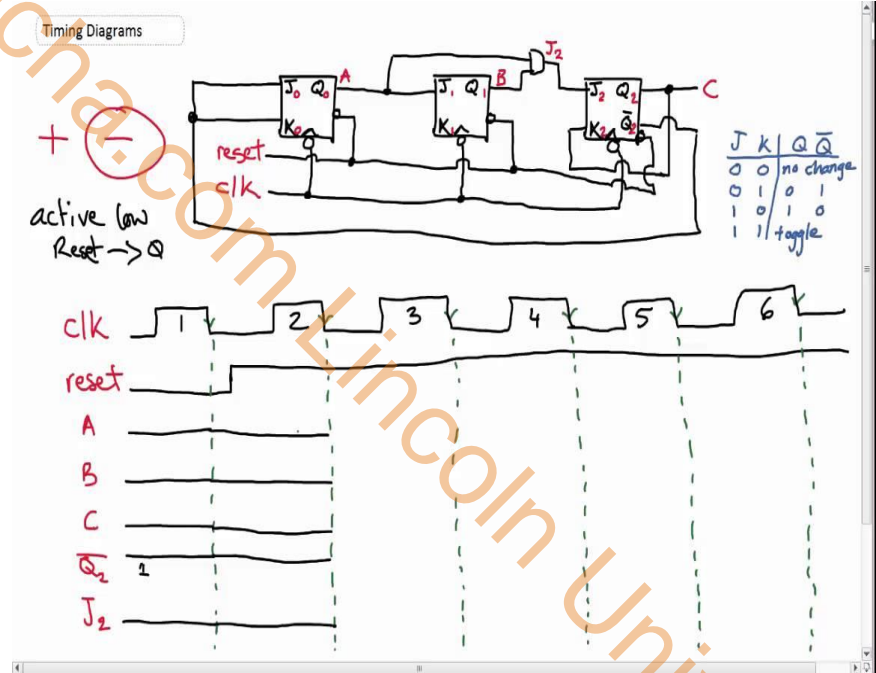By analyzing these diagrams, designers can ensure that the circuit meets timing constraints for reliable operation.



Design Considerations

When designing clocked sequential circuits, it's essential to consider propagation delays and setup/hold times.

Proper timing analysis can prevent issues such as race conditions and glitches.

Designers often use simulation software to verify the functionality and timing of their circuits before implementation.

Design Procedure for Clocked Sequential Circuits

Step 1: A State diagram or timing diagram is given, which describes the behaviour of the circuit that is to be designed.


Step 2: Obtain the state table.

Step 3: The number of states can be reduced by state reduction method.

Step 4: Do state assignment. (If required)

Step 5: Determine the number of flip-flops required and assign letter symbols.

 Step 6: Decide the type of flip-flop to be used.



167


Digital Electronics

Applications of Edge-Triggered Flip-Flops

Edge-triggered flip-flops are widely used in memory devices, where they store bits of information.

They are critical in creating registers, counters, and state machines in digital electronics.

 Their ability to synchronize data flow makes them indispensable in complex digital systems.



Conclusion

Understanding edge-triggered flip-flops and clocked sequential circuits is fundamental in digital design.

Their precise timing and state management capabilities enable the construction of reliable electronic systems.



Continuous advancements in technology further enhance their applications in modern digital devices.

Analysis of Clocked Sequential Circuits

★ T Flip-Flops

Example:

Present State		I/P	Next State		FF Inputs		O/P
A	B	x	A	B	T _A	T _B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	0
1	0	0	1	0	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	1

  

**UNIT 7: REGISTERS,
COUNTERS AND MEMORY
UNITS**

es:in:ad
com Lincoln University

Registers □ Ripple Counters □ Binary Ripple Counters


esikhcha.com Lincoln University

Introduction to Registers

Registers are small storage locations within a CPU that hold data temporarily.

They are crucial for the execution of instructions and help manage the flow of data within a computer.

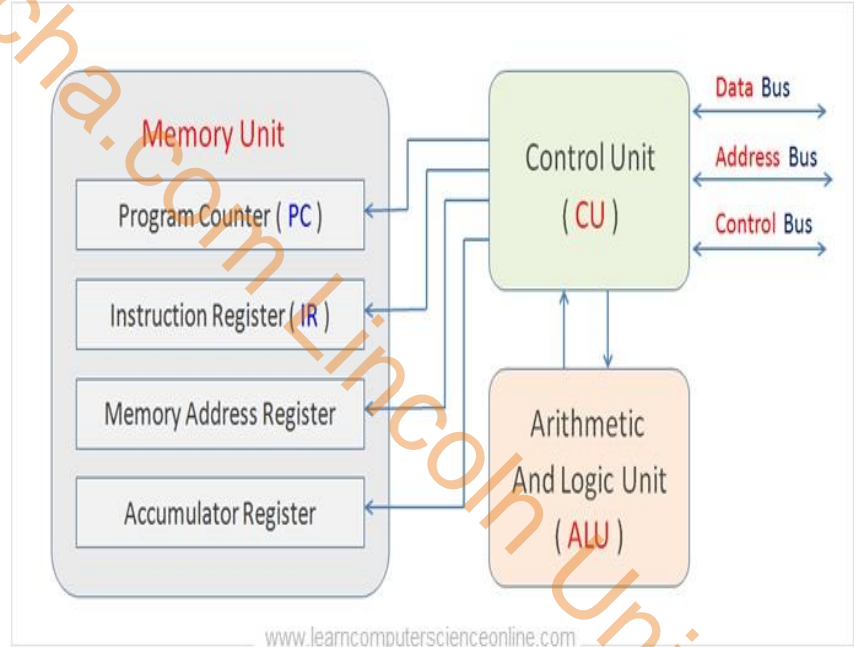Registers differ in size and functionality, with some designed for specific operations like arithmetic or control tasks.




Types of Registers

There are several types of registers, including general-purpose and special-purpose registers.

General-purpose registers can be used for various operations, while special-purpose registers serve specific functions.

 Examples of special-purpose registers include the Program Counter (PC) and the Stack Pointer (SP).



Introduction to Counters

Counters are sequential circuits that count pulses and can represent a series of binary states.

They are widely used in digital circuits for counting events, clock cycles, and frequency division.

Counters can be categorized into synchronous and asynchronous types based on their triggering mechanism.


1	0	0	0
1	0	0	0
1	0	0	0
1	0	0	0
0	1	1	1
0	1	1	1
0	1	1	1
0	1	1	1

Ripple Counters Overview

A ripple counter is an asynchronous counter where the flip-flop output serves as a clock for the next flip-flop.

The term "ripple" refers to the way the trigger signal propagates through the flip-flops.

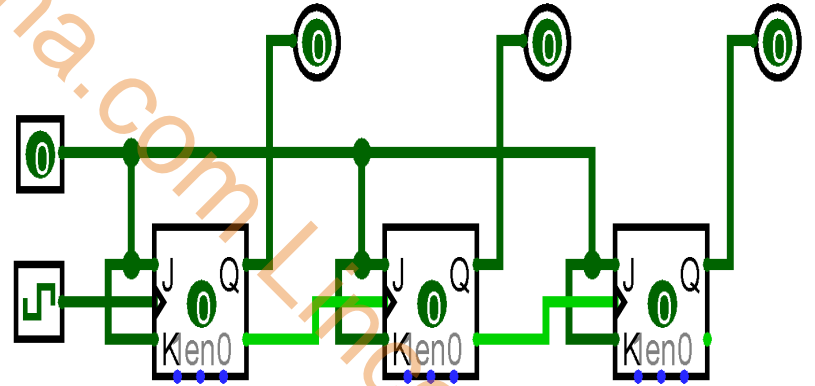Ripple counters are simpler in design but can introduce propagation delays due to the sequential triggering.



Asynchronous/Ripple Counter

Ripple Counter Operation

In a ripple counter, the first flip-flop toggles with each clock pulse.

Each subsequent flip-flop toggles based on the output of the previous flip-flop.

This cascading effect can lead to timing issues, particularly in high-speed applications.



esikhcha.com Lincoln University

Binary Ripple Counters

A binary ripple counter is a specific type of ripple counter that counts in binary sequence.

It typically consists of a series of flip-flops, with each flip-flop representing a bit of the binary number.

For example, a 3-bit binary ripple counter can count from 0 to 7 in binary format (000 to 111).


n-bit binary ripple counter

In a **ripple counter**, the carry information ripples from the less significant to the more significant bits.

Assume that the propagation delay from T to Q in the flip-flops on the right is 10ns.

How long do we have to wait after a clock input to read the value of the counter?

 Is the waiting time dependent on the modulus of the counter?




Advantages of Binary Ripple Counters


Binary ripple counters are easy to design and require fewer components compared to synchronous counters.

They are cost-effective for applications where high-speed operation is not critical.

 Ripple counters can be implemented using various types of flip-flops, such as T or JK flip-flops.



(a) Three-bit binary ripple counter

 

(b) Waveforms

Fig 8.1

Limitations of Binary Ripple Counters

The primary limitation of binary ripple counters is the propagation delay, which can limit counting speed.

As the number of bits increases, the cumulative delay becomes significant, affecting performance.

Additionally, ripple counters are less reliable in high-frequency applications due to timing uncertainties.


n-bit binary ripple counter

In a ripple counter, the carry information ripples from the less significant to the more significant bits.

Assume that the propagation delay from T to Q in the flip-flops on the right is 10ns.

How long do we have to wait after a clock input to read the value of the counter?

 Is the waiting time dependent on the modulus of the counter?




Applications of Binary Ripple Counters

Binary ripple counters are commonly used in digital clocks, frequency dividers, and event counters.

They are also found in applications requiring simple counting mechanisms without precise timing.

 Despite their limitations, they remain popular in educational settings for teaching digital electronics concepts.




Conclusion

Registers and ripple counters play essential roles in digital circuits and computer architecture.

Understanding binary ripple counters provides insights into asynchronous counting mechanisms and their applications.

 As technology advances, the relevance of these components continues, influencing design strategies in modern electronics.



Synchronous Counters ☐ Timing Sequences


esikhcha.com Lincoln University

Introduction to Synchronous Counters

Synchronous counters are digital devices that count in a specific sequence based on clock pulses.

They utilize flip-flops that are triggered simultaneously by the same clock signal.

 This coordinated timing allows for more accurate and predictable counting behavior compared to asynchronous counters.




Basics of Synchronous Counting

A synchronous counter changes its state simultaneously with each clock pulse.

The output of each flip-flop is connected to the clock input of the next flip-flop.

 This setup minimizes propagation delay, improving overall speed and performance.



esikhcha.com Lincoln University

Types of Synchronous Counters

Common types include binary counters, decade counters, and up/down counters.

Binary counters count in binary format, while decade counters count from 0 to 9.

Up/down counters can count in both increasing and decreasing order based on control signals.




Timing Sequences in Synchronous Counters

Timing sequences dictate how and when the counter increments its value.

The clock signal triggers transitions in the flip-flops, which define the counting sequence.

 Proper timing ensures that outputs reflect accurate counts in real-time applications.



Timing Diagram of 3-bit Synchronous Counter

Flip-Flop Operation

Flip-flops are the building blocks of synchronous counters, storing a single bit of data.

Each flip-flop changes state based on the clock signal and the input from the preceding flip-flop.

Understanding flip-flop behavior is crucial for designing effective synchronous counters.




Advantages of Synchronous Counters

Synchronous counters have faster operation due to simultaneous state changes.

They are less susceptible to glitches because all flip-flops are triggered by the same clock pulse.

 Their predictable timing sequences make them ideal for complex digital systems.




Asynchronous/Ripple Counter

Applications of Synchronous Counters

Synchronous counters are widely used in digital clocks, frequency dividers, and digital systems.

They serve as essential components in microcontrollers and digital signal processing devices.

 Their versatility allows them to be implemented in various fields, including telecommunications and automation.




Common Issues and Troubleshooting

Timing issues can arise if flip-flops do not operate within their specified parameters.

Glitches may occur if the clock signal is not stable or if setup and hold times are violated.

 Proper testing and validation techniques are essential to ensure the reliability of synchronous counters.




Conclusion

Synchronous counters provide a reliable method for counting in digital electronics.

Their timing sequences and operation principles are critical for designing efficient systems.

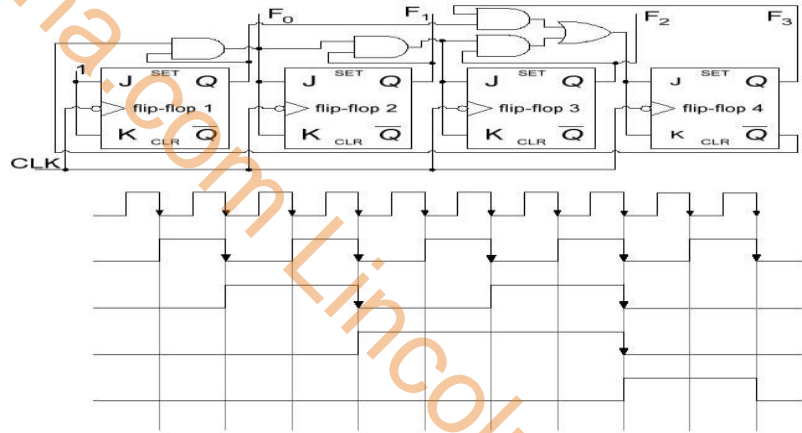Understanding their functionality and applications can enhance the design of modern digital circuits.



Johnson Counter \Rightarrow Memory Unit (RAM)

esikhcha.com Lincoln University

Introduction to Johnson Counter

The Johnson Counter, also known as the Twisted Ring Counter, is a type of digital counter.

It is a modified version of the ring counter that uses feedback to create a unique counting sequence.

Johnson Counters are widely used in digital circuits for their simplicity and efficiency in counting applications.


7. A switch-tail counter (also called twisted ring counter, Johnson counter) uses the complement of the serial output of a right shift register as its serial input.
 - (a) Starting from an initial state of 000, list the sequence of states after each shift until the register returns to 000.
 - (b) Beginning in state 00...0, how many states are there in the count sequence of an n -bit switch-tail counter?
 - (c) Design a decoder to be driven by the counter that produces a one-hot code output for each of the states. Make use of the don't-care states in your design.

Johnson Counter Operation

The Johnson Counter operates by shifting bits in a sequence that generates a specific pattern.

It utilizes flip-flops connected in a ring, with the output of the last flip-flop fed back to the input of the first.

 Each clock pulse results in a change in the state of the flip-flops, producing a predictable output sequence.



Characteristics of Johnson Counter

A Johnson Counter has a state sequence that is double the number of flip-flops used.

For example, a 3-bit Johnson Counter will have 6 unique states.

This characteristic makes it useful for applications requiring more states without increasing the number of flip-flops significantly.

Ring Counter

A ring counter is a typical application of the Shift register. The ring counter is almost the same as the shift counter. The only change is that the output of the last flip-flop is connected to the input of the first flip-flop in the case of the ring counter but in the case of the shift register it is taken as output. Except for this, all the other things are the same.

No. of states in Ring counter = No. of flip-flop used

So, for designing a 4-bit Ring counter we need 4 flip-flops.

Ring Counter

In this diagram, we can see that the clock pulse (CLK) is applied to all the flip-flops simultaneously. Therefore, it is a Synchronous Counter. Also, here we use Overriding input (ORI) for each flip-flop. Preset (PR) and Clear (CLR) are used as ORI. When PR is 0, then the output is 1. And when CLR is 0, then the output is 0. Both PR and CLR are active low signal that always works in value 0.

PR = 0, Q = 1
CLR = 0, Q = 0

These two values are always fixed. They are independent of the value of input D and the Clock pulse (CLK).

Working –

	PR	CLR	D	Q
low	X	1	0	0
high	low	0	1	0
high	low	0	0	1
high	low	0	0	0
high	low	1	0	0


Initially a low clear (CLR) pulse is applied to all flip-flops. Hence FF-3, FF-2, FF-1 will be reset but FF-0 will be set. So outputs are:

Applications of Johnson Counter

Johnson Counters are commonly used in digital clocks, frequency dividers, and LED chasers.

They are ideal for applications requiring a simple and reliable counting mechanism.

 Additionally, they can be found in shift registers and digital signal processing systems.




Introduction to Memory Unit (RAM)

RAM, or Random Access Memory, is a type of volatile memory used in computers and devices.

It allows data to be read and written in any order, making it essential for system performance.

 RAM temporarily stores data that the CPU needs while executing tasks and running applications.




Types of RAM

There are primarily two types of RAM: Static RAM (SRAM) and Dynamic RAM (DRAM).

SRAM is faster and more reliable but is also more expensive and consumes more power.

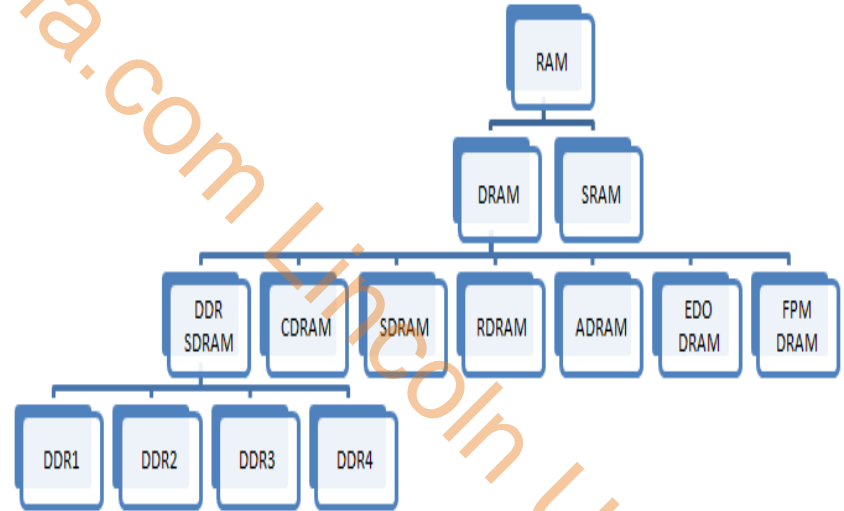In contrast, DRAM is slower, less expensive, and requires periodic refreshing to maintain data.




Working Principle of RAM

RAM operates by using memory cells made up of transistors and capacitors to store data.

When data is written to RAM, it is stored as an electrical charge in these cells.

 The CPU can access this data almost instantaneously, allowing for quick data retrieval and processing.




Importance of RAM in Computing

RAM is critical for multitasking, as it allows several applications to run simultaneously without lag.

The amount of RAM in a system directly impacts its performance and speed.

 Upgrading RAM can lead to significant improvements in overall system responsiveness and capability.




Future Trends in RAM Technology

Emerging technologies like DDR5 and LPDDR5 are set to enhance RAM speeds and efficiency.

Innovations in memory design, such as 3D NAND and memory stacking, are also being explored.

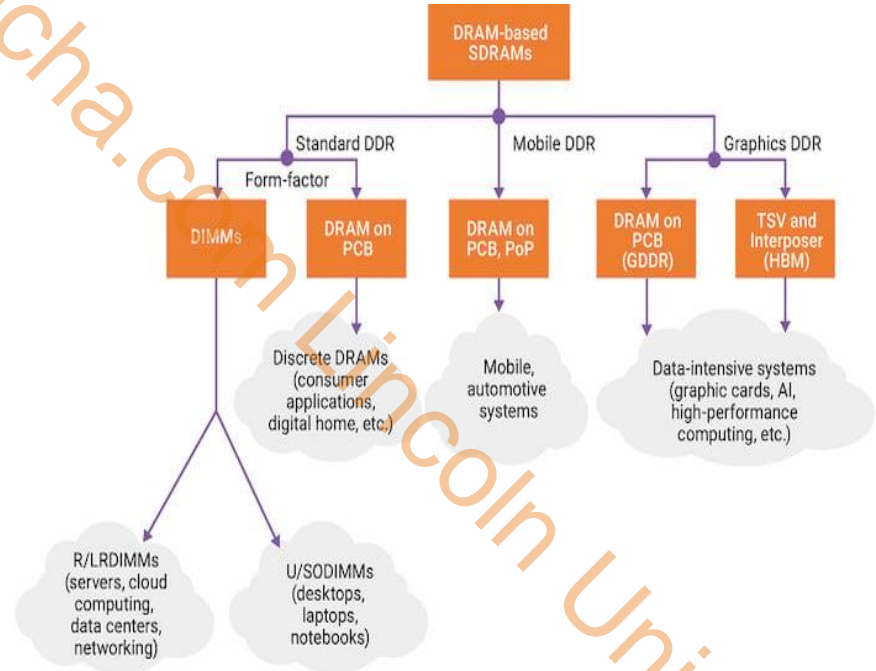These advancements aim to meet the increasing demands for higher performance in computing and gaming.



Conclusion

Both the Johnson Counter and RAM play crucial roles in digital electronics and computing.

Understanding their functions and applications is essential for anyone involved in technology.

As technology evolves, the importance of efficient counting mechanisms and memory solutions continues to grow.

esikhcha.com Lincoln University